

APPLICATION NOTE 1071

# DAC-Powered Charge Pump Varies Negative Rail

The circuit shown in **Figure 1** provides a low-current, adjustable negative supply rail suitable for use as a sensor bias, liquid-crystal-display (LCD) contrast bias, or voltage-controlled-oscillator (VCO) tuning supply. By operating a charge-pump doubler from the output of a buffered digital-to-analog converter (DAC), the circuit avoids the customary approach involving clumsy level shifters based on op amps and discrete components.

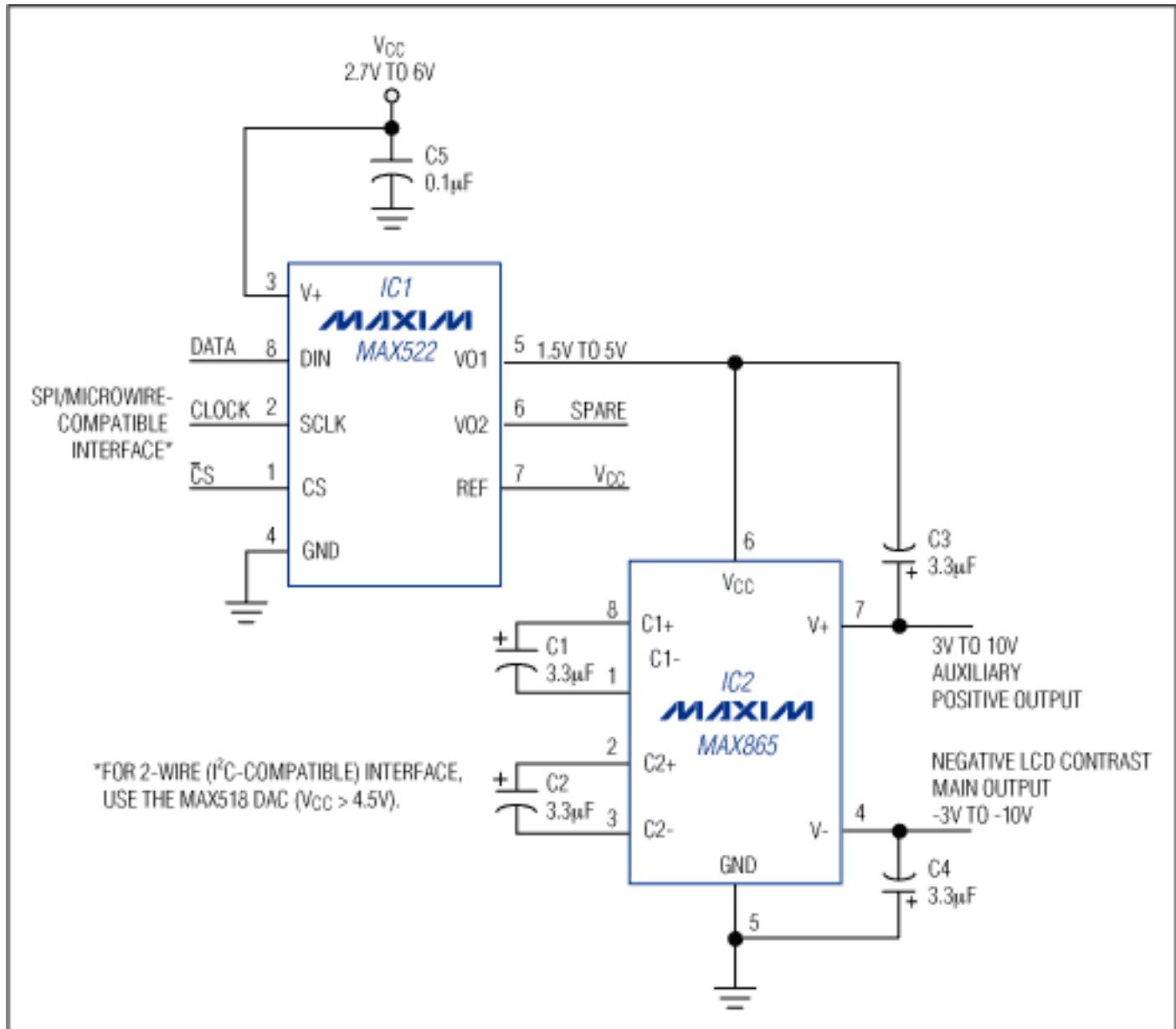


Figure 1. This adjustable negative supply consists of an inverting-doubler charge pump controlled by an 8-bit, serial-input DAC.

IC1 is a dual, 8-bit DAC with serial input and buffered voltage outputs. Output impedances are 50Ω; therefore, the DAC output in use drops about 50mV while providing the 1.1mA typically drawn by the IC2 charge pump. As the input code varies from 0 to 255, the DAC output ranges rail-to-rail, changing approximately 40mV per step.

With a +5V input ( $V_{CC}$ ) applied to IC1 and a -3V output from IC2, the code that produces the minimum allowable voltage to the charge pump (1.5V) is 80 (decimal). The charge pump draws 0.6mA and generates  $\pm 2$  times the voltage at its  $V_{CC}$  terminal, producing  $\pm 3V$  to  $\pm 12V$  as its input ranges from 1.5V to 6V. (The positive and negative outputs can be used simultaneously.) The main power can go as low as 2.7V, producing a negative output slightly over -5V. The minimum code for this condition is about 140 (decimal).

To shut down the supply, simply write zeros to the DAC. The DAC itself has a shutdown mode that draws only 1 $\mu$ A. To ensure a reliable start-up when bringing the system out of shutdown, write a value that powers the charge pump with a minimum of 2V. Note that a microcontroller ( $\mu$ C) with a pulse-width-modulation (PWM) output can eliminate the DAC altogether. For example, you can provide a variable  $V_{CC}$  to the charge pump by filtering a 20kHz PWM signal with a 270 $\Omega$ /3.3 $\mu$ F lowpass network. Be sure the  $\mu$ C's port pin can supply the current with an acceptable voltage drop; if not, buffer it with a CMOS buffer or inverter such as the 74HC04.

*A related idea appeared in the 7/21/97 issue of Electronic Design.*

---

Application Note 1071: <http://www.maxim-ic.com/an1071>

### More Information

For technical questions and support: <http://www.maxim-ic.com/support>

For samples: <http://www.maxim-ic.com/samples>

Other questions and comments: <http://www.maxim-ic.com/contact>

### Related Parts

MAX522: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX552: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX865: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN1071, AN 1071, APP1071, Appnote1071, Appnote 1071

Copyright © by Maxim Integrated Products

Additional legal notices: <http://www.maxim-ic.com/legal>