

APPLICATION NOTE 110

# Boost Converter Has High Efficiency At Light Loads

In most DC-DC converters, the normal supply currents do not allow high efficiency at low load currents. The circuit in **Figure 1**, however, contains micropower components that enable it to maintain 90% efficiency for load currents as low as 1mA. IC1 (a quad Schmitt-trigger NAND gate) draws maximum quiescent currents of only 0.25µA, and IC2 (a combination voltage reference and comparator) draws only 2.5µA.

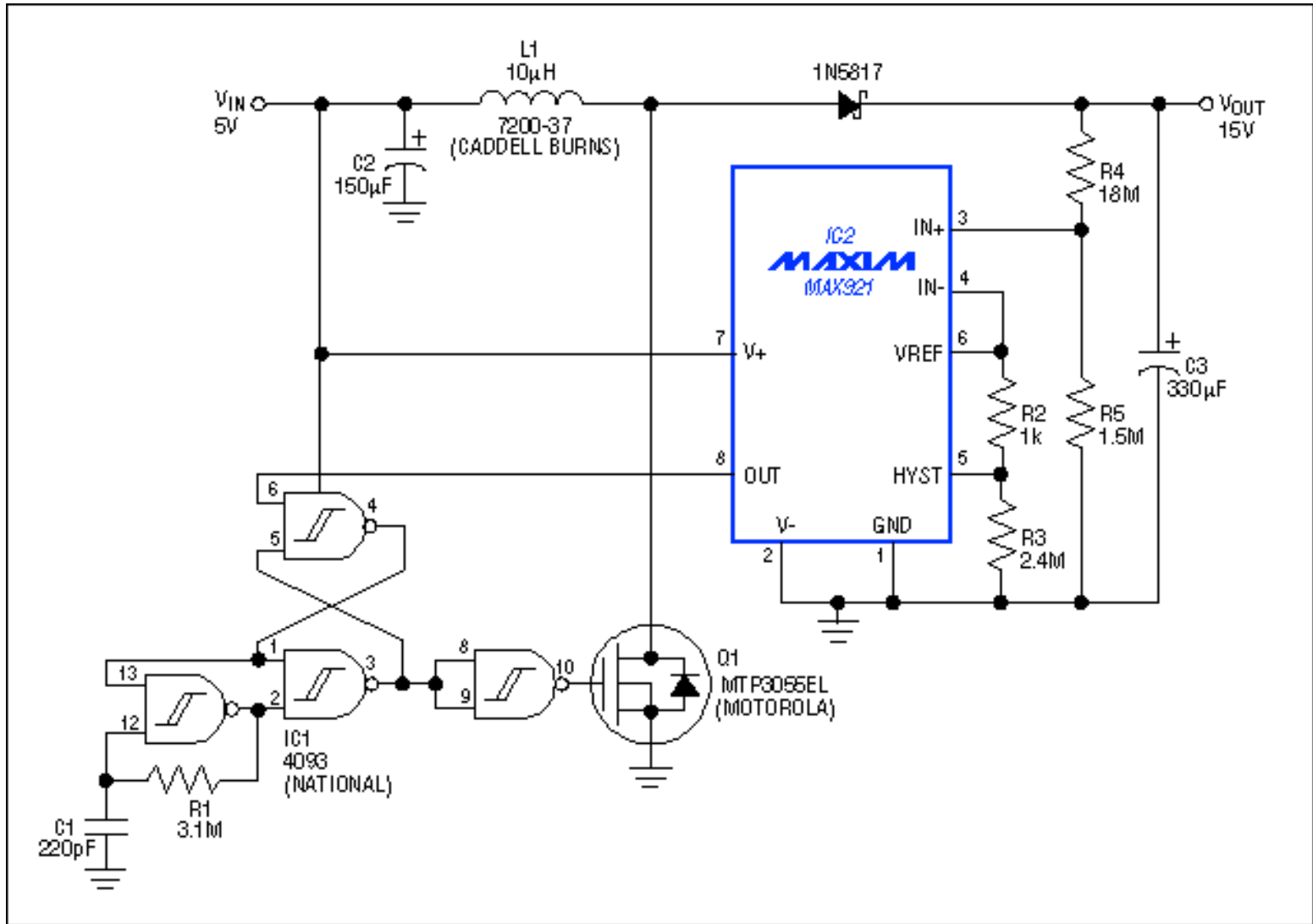


Figure 1. Consuming only microwatts of power, this 5V-to-15V boost converter provides low load currents with high efficiency.

IC2 compares its own reference voltage against the circuit output,  $V_{OUT}$ . The resulting comparator output (pin 8) is high when  $V_{OUT}$  is above its threshold and low otherwise. The quad NAND gate is configured as an oscillator, a set/reset latch, and a buffer inverter. The latch blocks oscillator pulses when the comparator output is high. When it goes low, the pulses pass through to Q1's gate and activate the boost regulator.

R4 and R5 help determine the circuit's DC output level:  $V_{OUT} = V_{REF}(1 + R4/R5)$ . The output voltage ripple for light loads depends on the comparator's hysteresis. With  $R3 = 2.4M\Omega$ , the hysteresis in millivolts equals the value of R2 in kilohms. Then, the ripple in millivolts equals  $V_{REF}(1 + R4/R5)(R2)$ , where R2 is in kilohms. For this circuit, ripple =  $1.182V(1 + 18/1.5)(1) = 15.4mV$ .

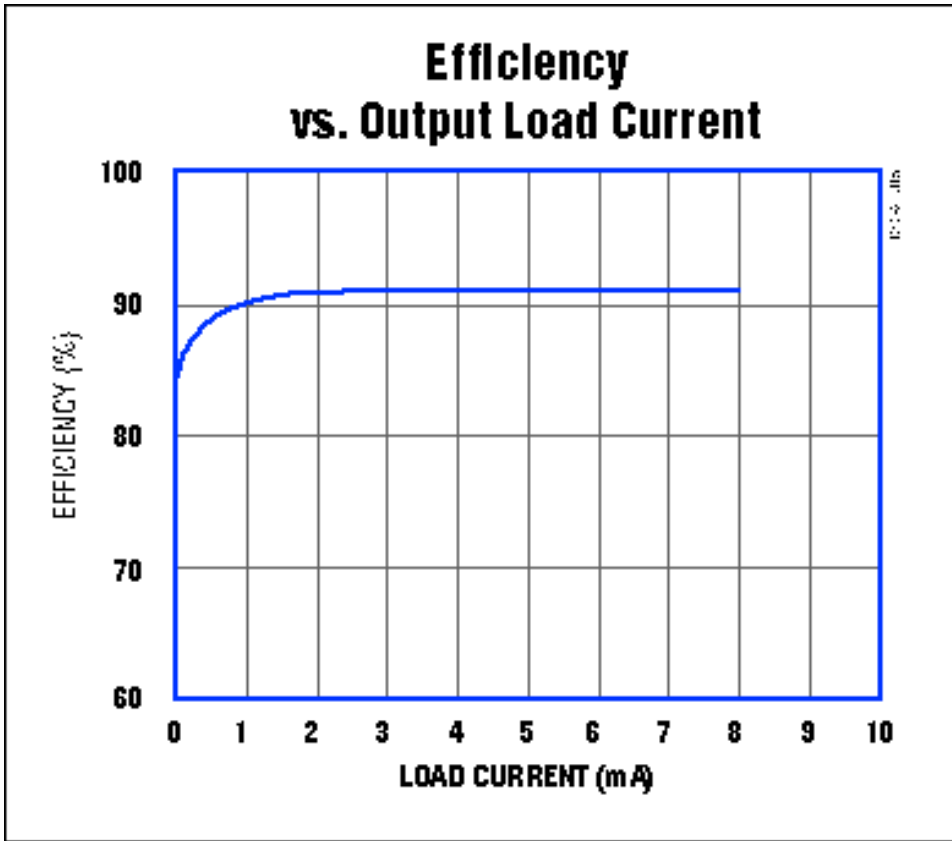


Figure 2. Efficiency in the Figure 1 circuit exceeds 90% for load currents between 1mA and 8mA.

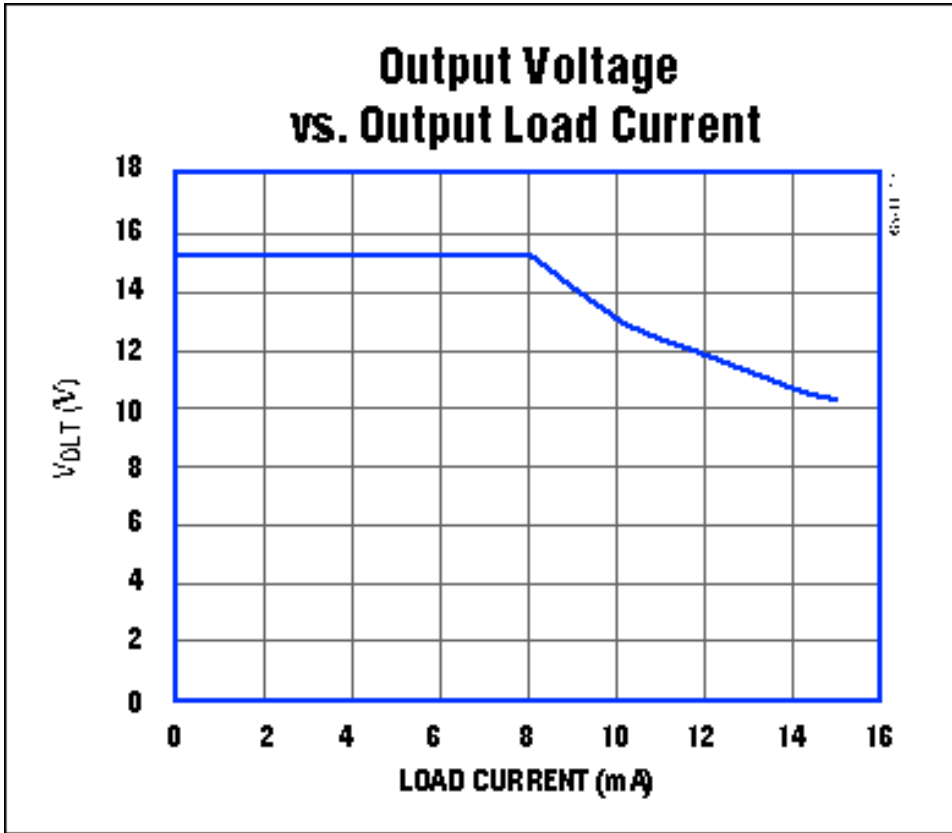


Figure 3. The oscillator frequency in Figure 1, set low to conserve power, also sets a sharp limit on load current.

For technical questions and support: <http://www.maxim-ic.com/support>

For samples: <http://www.maxim-ic.com/samples>

Other questions and comments: <http://www.maxim-ic.com/contact>

### **Related Parts**

MAX921: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN110, AN 110, APP110, Appnote110, Appnote 110

Copyright © by Maxim Integrated Products

Additional legal notices: <http://www.maxim-ic.com/legal>