



APPLICATION NOTE 1161

Current Limited DC-DC Controller Used as Step-Up Step-Down SEPIC Power Supply for USB Devices

Abstract: USB powered devices require a regulated supply. Unfortunately, the USB bus voltage can vary from 4V to 9V. Configuring the MAX668 boost controller into step-up/step-down topology can generate a current-limited regulated supply.

Universal Serial Bus (USB) is a popular way to connect PCs and consumer devices. It is simple and inexpensive and can connect multiple external peripherals simultaneously. As mobile devices add more functionality such as text messaging, web surfing, information storage and music playing, the need to communicate with a PC is increasing. Many of the mobile devices today offer a USB interface native in the device. The sole purpose is to provide a connection for data communication. The device may be self powered (e.g., through a wall adapter) or draw the power from the USB bus.

The mobile devices are typically expected to connect to a powered USB hub. A USB device can have its own power source (e.g. batteries or a wall plug) or draw the power from the USB bus. A powered USB host can provide up to 500mA current. Using the power supplied by USB can be tricky because the voltage to a USB powered device may be as low as 4.35V, when cable and connector drops are considered, or as high as 5.5V. If the device is to operate with a voltage adapter for a source it may see input voltages as high as 9V. In order to accommodate these various scenarios, a step-up/step-down DC-DC topology works well. The input and output specifications for a controller/converter are summarized in Table 1.

Table 1. Power Supply Requirements for USB Compatible Portable Device

Parameter	Requirement
Input Voltage V_{IN}	4V to 9V
Input Current I_{IN}	500mA ($\pm 5\%$) max.
Output Power P_{OUT}	2.4W typical
Output Voltage V_{OUT}	6V ($\pm 5\%$) typical
Output Load Current I_{OUT}	400mA max.
Regulation	Min. $V_{OUT} = 5.5V$ at $I_{OUT} = 200mA$

SEPIC to 6V with Input Current Limiting

This step-up/step-down supply is used to power a Li+ battery charger. Since the charger itself will have a drop in voltage across it, the output voltage was set to 6V. The single-ended primary inductance converter shown in Figure 1 is ideal for this application. This buck-boost topology is needed since the input voltage can vary from values below the output voltage to values greater than the output voltage (Table 1). The MAX668 boost controller is adapted to SEPIC topology (**Figure 1**).

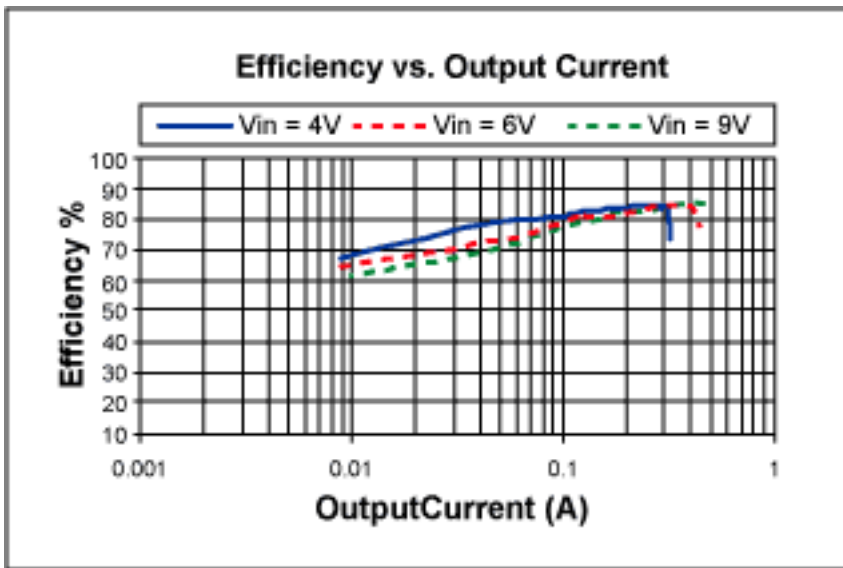


Figure 3. Efficiency of the MAX668 SEPIC.

Application Note 1161: <http://www.maxim-ic.com/an1161>

More Information

For technical questions and support: <http://www.maxim-ic.com/support>

For samples: <http://www.maxim-ic.com/samples>

Other questions and comments: <http://www.maxim-ic.com/contact>

Related Parts

MAX668: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN1161, AN 1161, APP1161, Appnote1161, Appnote 1161

Copyright © by Maxim Integrated Products

Additional legal notices: <http://www.maxim-ic.com/legal>