

APPLICATION NOTE 1213

Tracking Power Supply Has Dual Outputs

Designing a stable bipolar supply for powering op-amps, multiplexers, switches, etc. can be difficult, especially if the two voltages must track each other with respect to a non-zero or adjustable reference level. Such a regulated supply for low-power applications (**Figure 1**) produces a main-controller output voltage (V_{MAIN}) and two tracking voltages symmetric about an adjustable reference voltage (V_{REF}). You create the circuit by adding four Schottky diodes (D2-D5) and two flying capacitors (C2-C3) to the basic boost-converter circuit for U1.

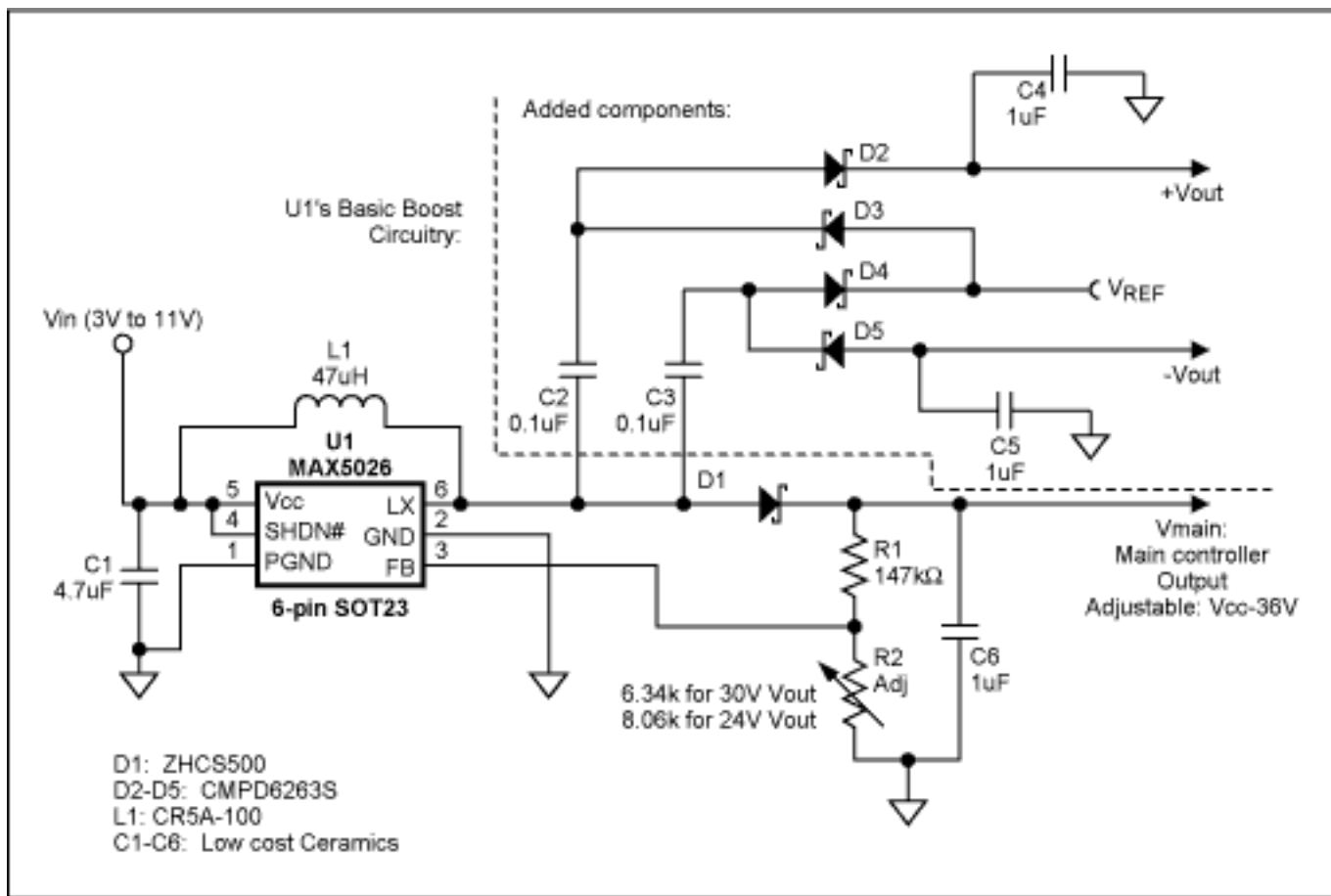


Figure 1. This single-IC circuit generates the bipolar voltages required in many industrial analog applications, as well as contrast-control voltages for an STN LCD.

U1 is an efficient, single-output boost converter for applications requiring outputs up to 36V and a wide input-voltage range (3V to 11V). U1 requires no external switching devices and draws a typical supply current of only 350μA, making it ideal for handheld and point-load applications. It is characterized for loads up to 120mW.

The ±30V outputs are centered about a reference level of $V_{REF} = 0V$ (**Figure 2**). For balanced loads of 0.5mA to 2mA, tracking is excellent over a wide input range. **Figure 3** shows how $+V_{OUT}$ and $-V_{OUT}$ track each other as V_{REF} is moved away from 0V. One example of the need for a non-zero V_{REF} is indicated in **Figure 4**, in which the

LCD-contrast voltages must be symmetric about V_{REF} to avoid a DC component across the liquid crystal, which in turn can damage the LCD or shorten its life.

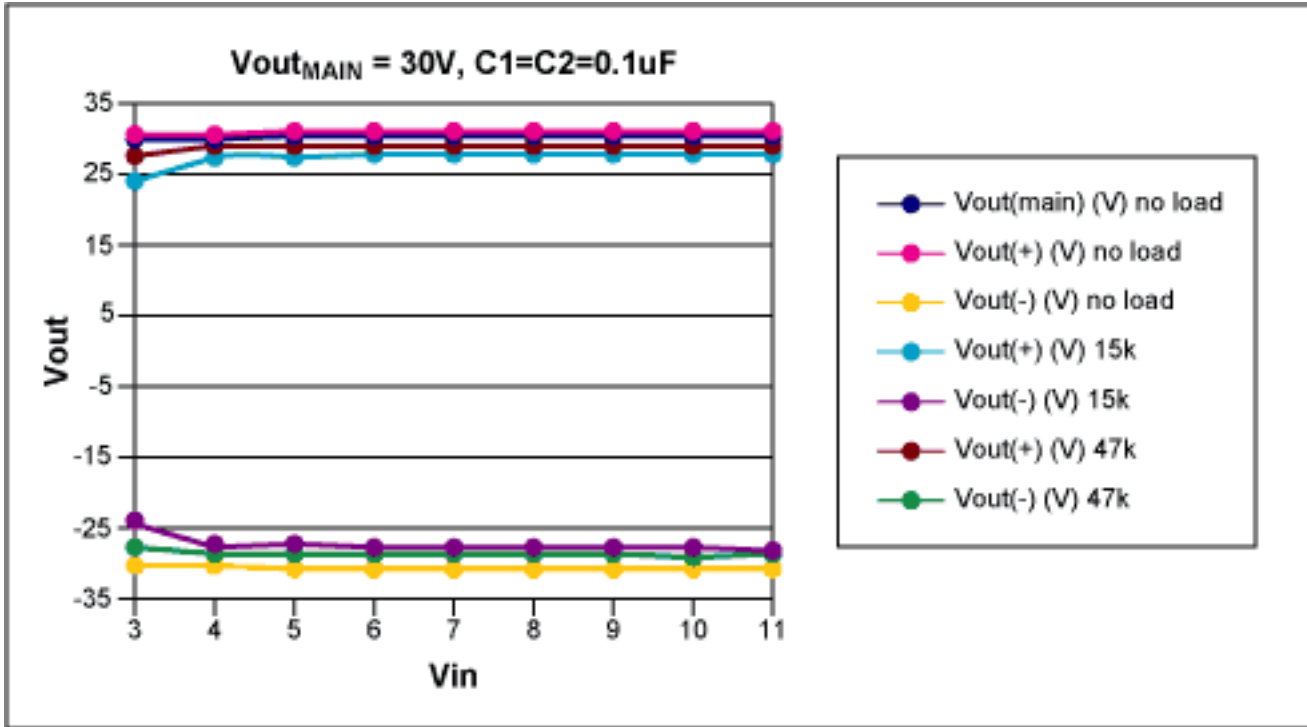


Figure 2. This graph shows the Figure 2 outputs of $\pm V_{OUT}$ and V_{MAIN} across the full 3V-11V input voltage range, under varying load conditions.

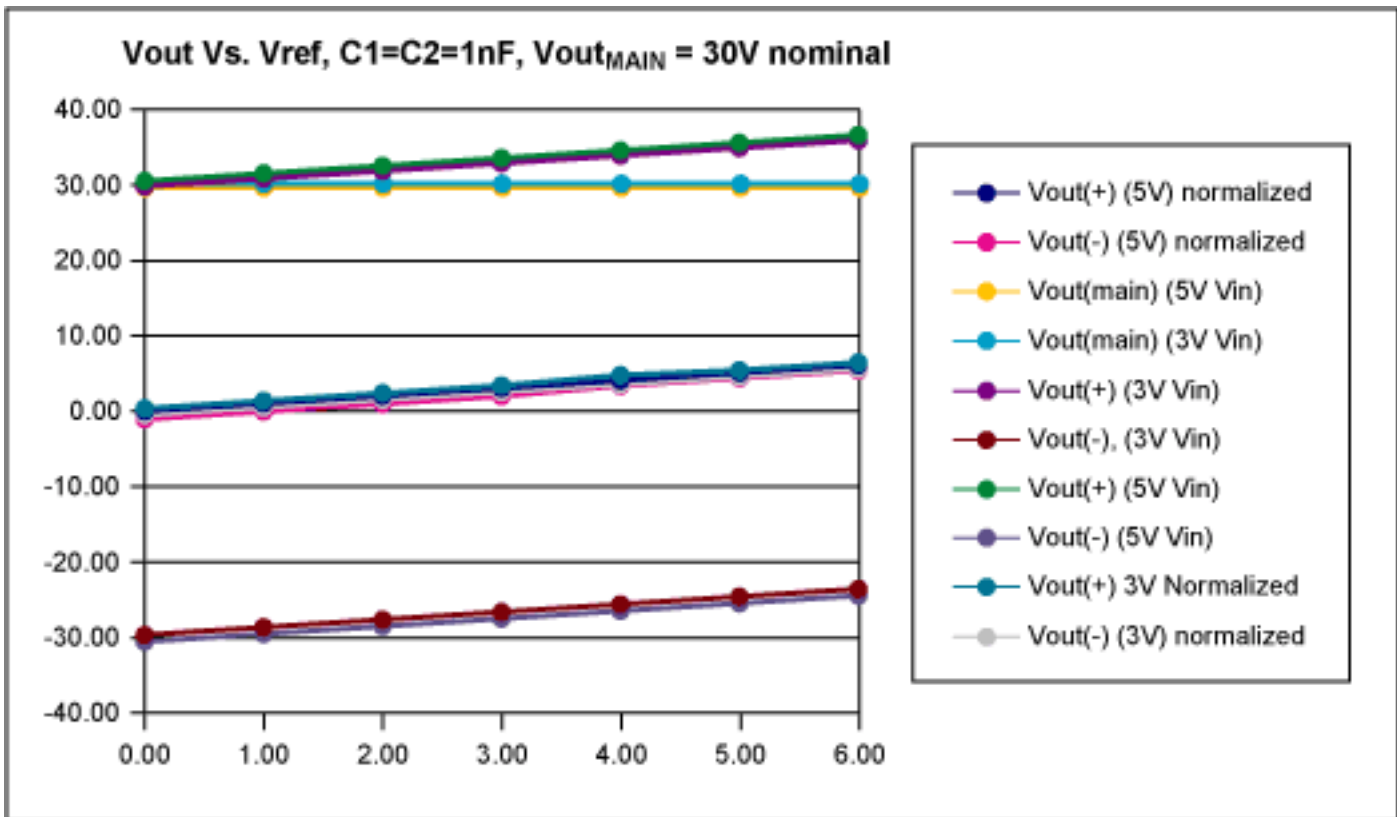


Figure 3. This graph shows that the $\pm V_{OUT}$ outputs in Figure 1 track each other with respect to changes in the reference voltage: $\pm V_{OUT} = V_{REF} \pm V_{MAIN}$.

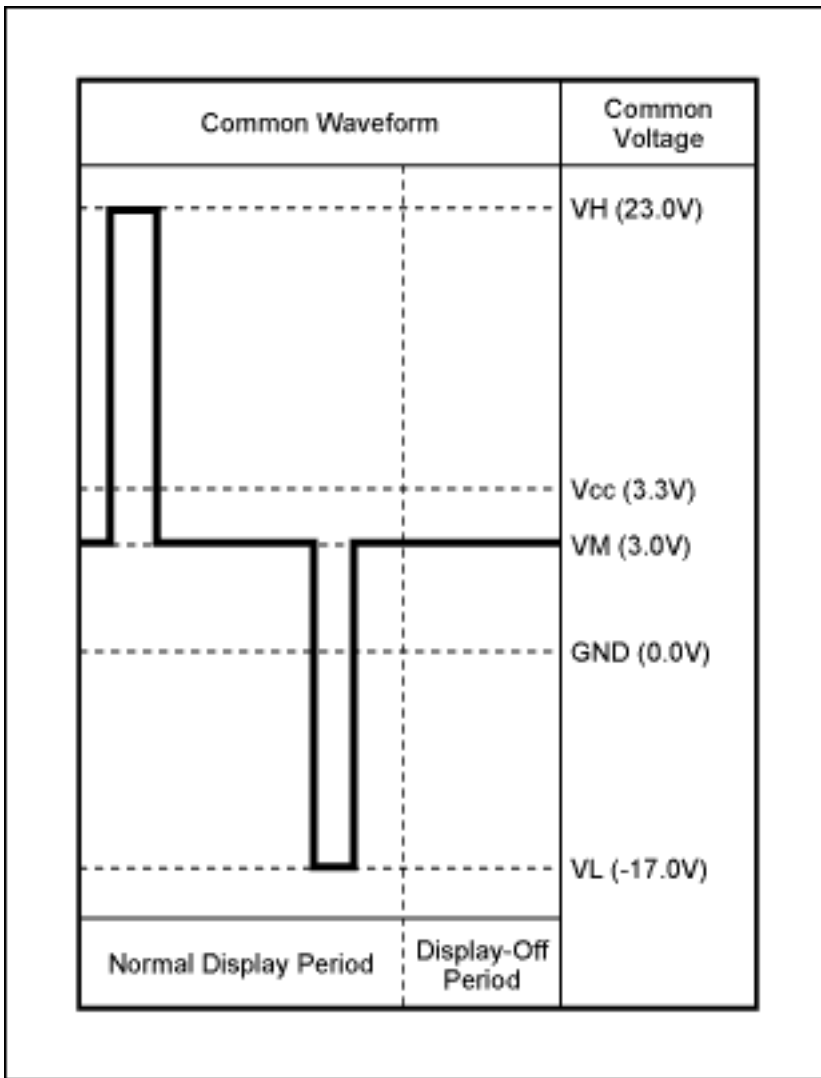


Figure 4. To avoid a damaging DC component across the LCD, these contrast waveforms are symmetrical about the reference level V_{REF} .

A FET internal to U1 repeatedly connects LX (pin 6) to ground and then releases it, causing the LX voltage to toggle between ground and V_{MAIN} plus one diode drop (D1). That action generates the $\pm V_{OUT}$ voltages as follows:

- V_{OUT} output, phase 1: The rise of LX voltage to $V_{OUT} + V_{DIODE}$ forces voltage on the other side of C3 to $V_{REF} + V_{DIODE}$, creating a differential of $V_{MAIN} - V_{REF}$ across C3. The LX node is our reference point. Phase 2: As LX is switched to ground, the load side ($-V_{OUT}$) sees $-V_{MAIN} + V_{REF}$, forcing current from the $-V_{OUT}$ load through D5, and the cycle repeats itself. Note that $+V_{OUT}$ and $-V_{OUT}$ develop on alternate phases. The resulting $-V_{OUT}$ voltage is

$$-V_{OUT} = -V_{MAIN} + V_{REF} + V_{DIODE}$$

+ V_{OUT} output, phase 2: When LX is switched to ground, the load side of C2 sees $V_{REF} - V_{DIODE}$. Then, (phase 1) the rise of LX to $V_{MAIN} + V_{DIODE}$ forces a voltage of $V_{MAIN} + V_{REF}$ on the other side of C2. The resulting $+V_{OUT}$ voltage is:

$$+V_{OUT} = V_{MAIN} + V_{REF} - V_{DIODE}$$

These load equations suggest, and Figures 2 and 3 illustrate, that $-V_{OUT}$ and $+V_{OUT}$ track each other with respect to V_{MAIN} , and are offset by one diode drop from V_{REF} . D1-D5 are low-current Schottky diodes. C2 and C3 can be ceramic capacitors in the range 1nF to 100nF, preferably with voltage ratings of approximately $2 \cdot |V_{OUT}|$. Larger values of C2 and C3 provide more stable outputs under a wide range of load currents. L1 is typically 47 μ H, and the output capacitors C4-C6 (shown with 1 μ F values) may be sized according to the allowable output ripple.

A similar version of this article appeared in the July 15, 2002 issue of *Planet Analog* magazine.

Application Note 1213: <http://www.maxim-ic.com/an1213>

More Information

For technical questions and support: <http://www.maxim-ic.com/support>

For samples: <http://www.maxim-ic.com/samples>

Other questions and comments: <http://www.maxim-ic.com/contact>

Related Parts

MAX5026: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN1213, AN 1213, APP1213, Appnote1213, Appnote 1213

Copyright © 2005 by Maxim Integrated Products

Additional legal notices: <http://www.maxim-ic.com/legal>