

APPLICATION NOTE 1789

A Cheap, Tiny LDO Provides Up To 2A Output Current

The MAX8515 programmable shunt regulator with a 0.6V feedback threshold features $\pm 0.5\%$ initial accuracy and a tiny 5-pin SC70 package. It can be used to build a cheap and tiny LDO using just an external NPN transistor and a few small external components. **Figure 1** shows the LDO circuit.

The input voltage ranges from 1.2V to 2.5V. The output voltage is 1.0V. The supply voltage for MAX8515 is 2.5V. The output current can be up to 2A.

The LDO circuit uses no output capacitors. This is possible because the compensation of the feedback loop of the LDO is separated from its output and the MAX8515 error amplifier has a wide bandwidth (800kHz zero cross frequency with 1 μ F compensation capacitor, C2). Therefore, small output ripple voltage and fast step load transient response can be achieved without the output capacitors.

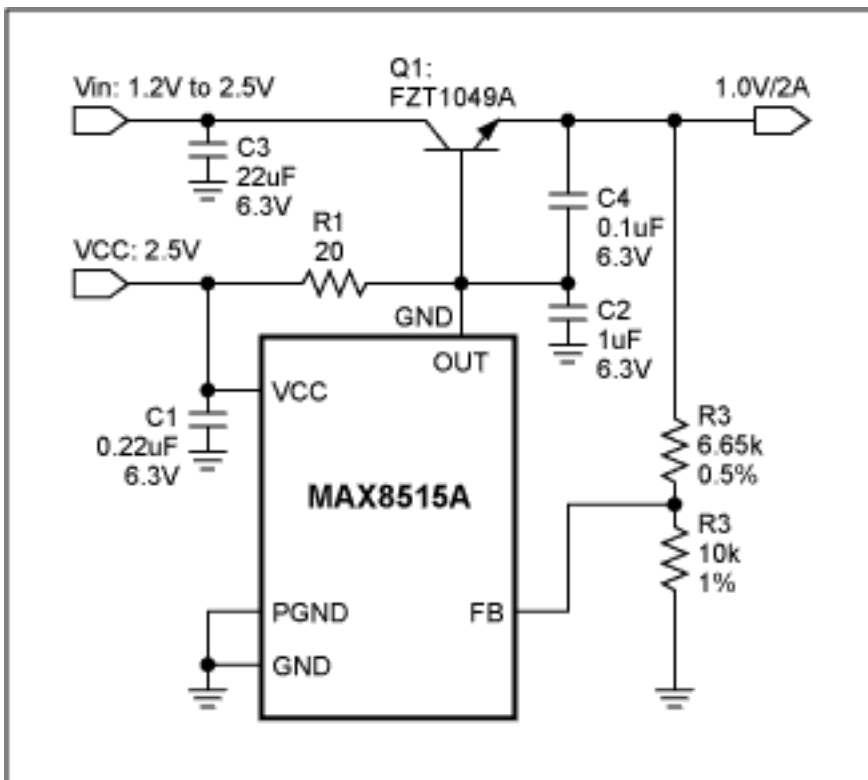


Figure 1. Schematics of a cheap and tiny LDO circuit using the MAX8515.

Figure 2 shows the step load transient response with 1.5A step load current (75% step load change). The transient response finishes within 4 μ s. For 25% step load change the maximum voltage deviation would be less than 40mV, meeting the $\pm 5\%$ requirement at 1.0V output.

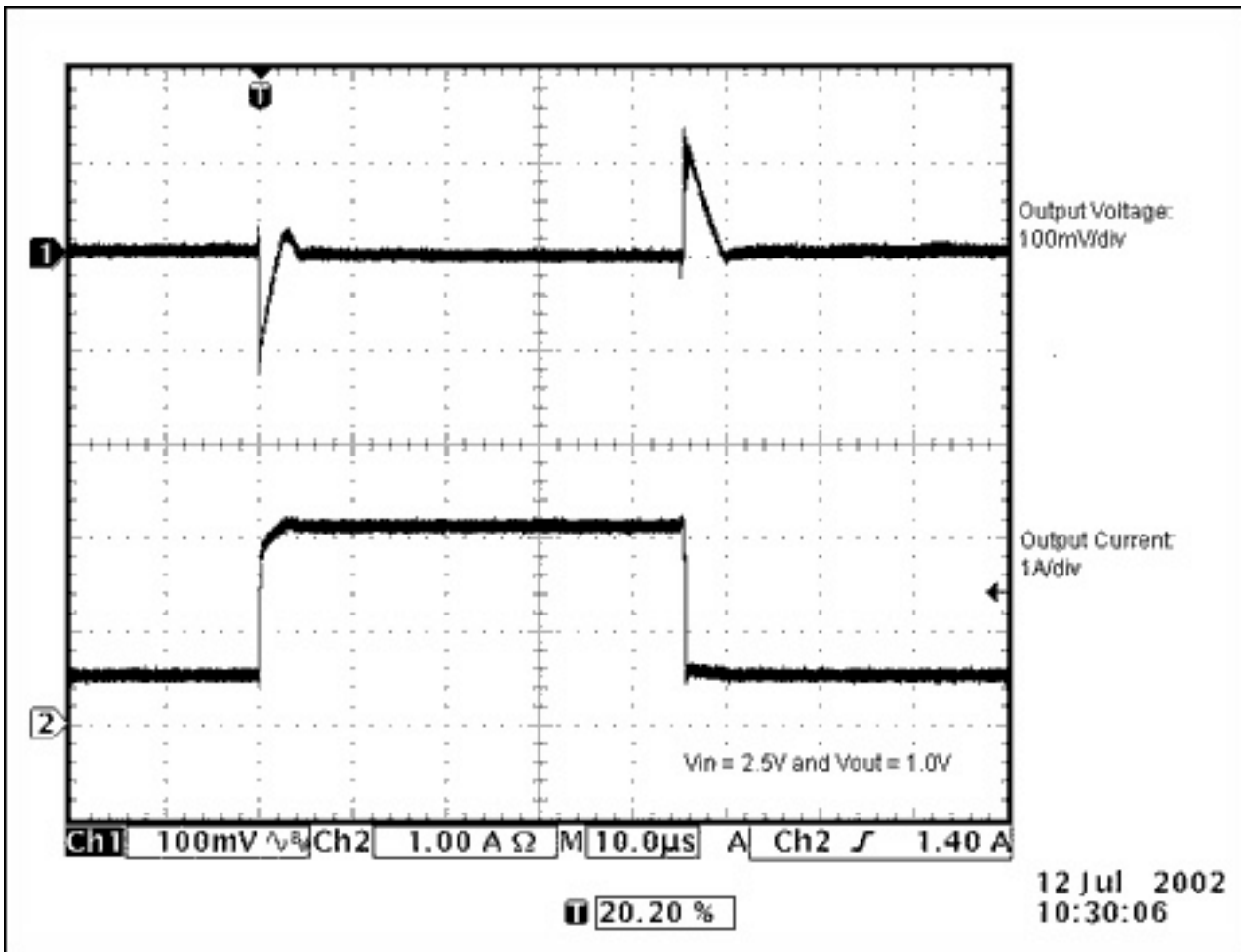


Figure 2. Step load transient response from 0.5A to 2.1A and back to 0.5A.

Figure 3 shows the output ripple voltage at 2.5V input and 2A of load current, where the peak-to-peak ripple voltage is less than 3mV.

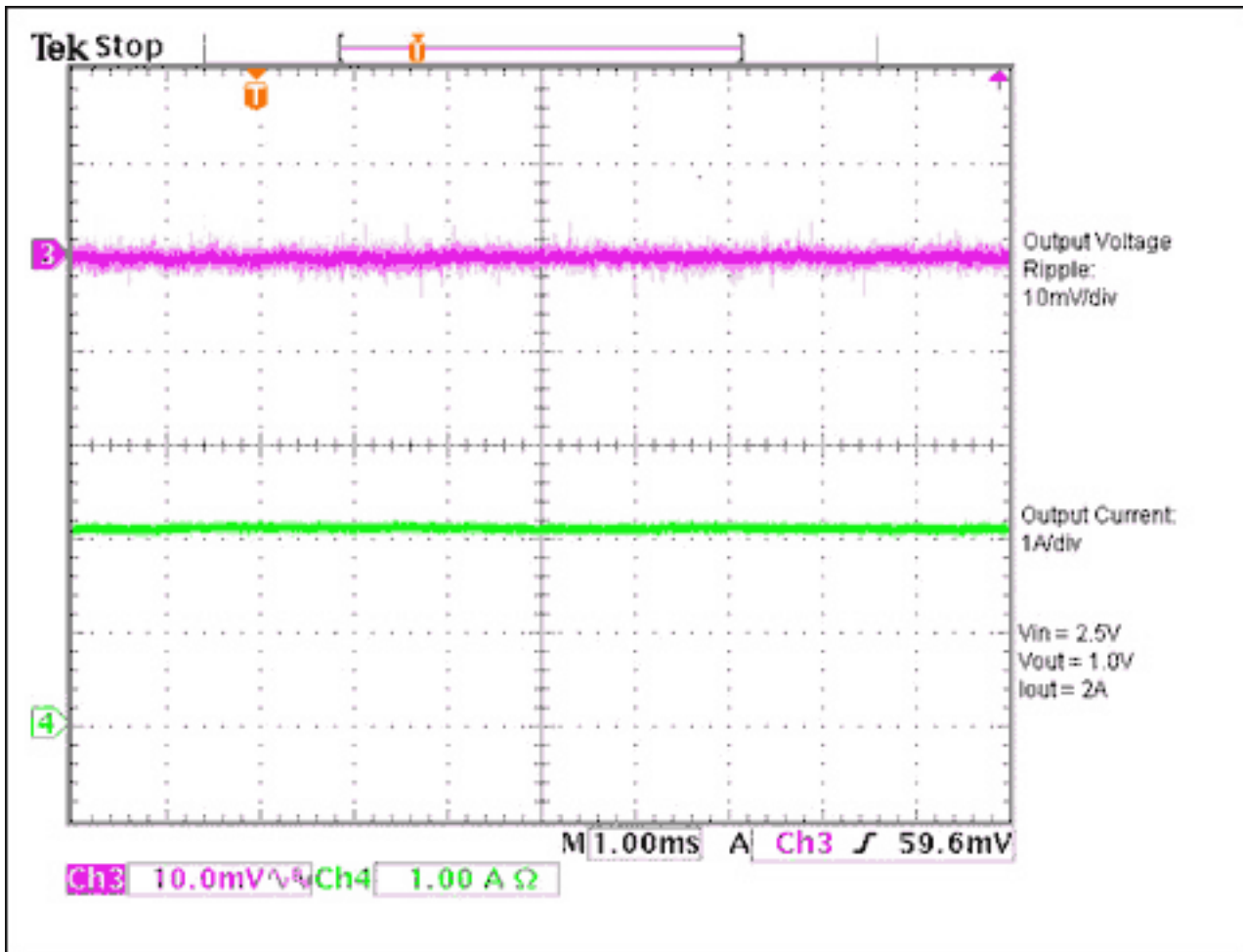


Figure 3. Output ripple voltage at 2A load current 2.5V input voltage.

It should be pointed out that the LDO shown in Figure 1 does not provide either short circuit or over load protection. Therefore it is recommended that the LDO be used as a post regulator after a DC-DC converter, which can provide short circuit protection. The tiny footprint and low cost make the LDO attractive where the board space and cost are especially important.

Application Note 1789: www.maxim-ic.com/an1789

More Information

For technical questions and support: www.maxim-ic.com/support

For samples: www.maxim-ic.com/samples

Other questions and comments: www.maxim-ic.com/contact

Keep Me Informed

Preview new application notes in your areas of interest as soon as they are published. Subscribe to [EE-Mail - Application Notes](#) for weekly updates.

Related Parts

MAX8515: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN1789, AN 1789, APP1789, Appnote1789, Appnote 1789

Copyright © by Maxim Integrated Products

Additional legal notices: www.maxim-ic.com/legal