

APPLICATION NOTE 1861

Pass Transistor Boosts Current from Negative Linear Regulator

Abstract: The addition of a pass transistor to the circuit of Figure 1 allows the linear regulator (LDO) to deliver more current to the load. A detailed power dissipation analysis is included to assist circuit developers in choosing the proper power rating of each component. Furthermore, lab data shows that the device is stable across temperature, line, and load.

Adding four components to a negative linear regulator (U1 in **Figure 1**) increases the allowable load current by 60%. Cost for the components is less than \$0.17 in 1k quantities.

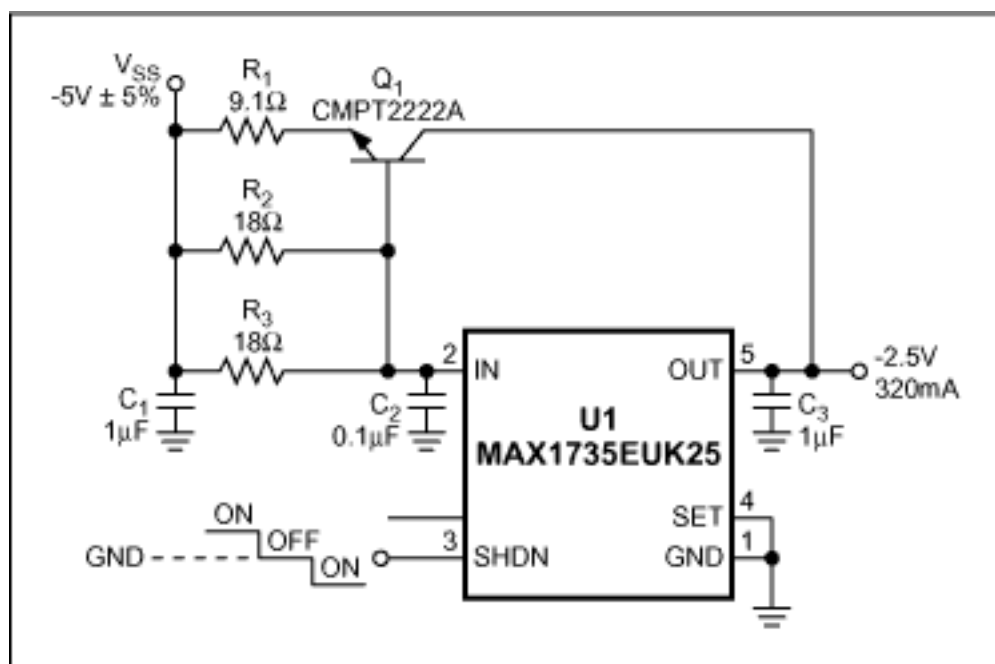


Figure 1. A pass transistor and associated resistors boosts load current in this negative linear regulator by 60%.

Connecting the SET terminal to ground sets U1's output voltage to -2.5V. U1's maximum load current is 200mA, and the extra components (Q₁, R₁, R₂, and R₃) draw another 120mA maximum from the load, producing (without degrading the output regulation) a total maximum load current of 320mA.

R₁ reduces the power dissipated in Q₁, prevents thermal runaway in Q₁, and provides momentary protection against short-circuited outputs. It also prevents oscillation by limiting gain in the Q₁ loop. Current flowing through U1 from OUT to V_{SS} produces a voltage drop of V_{R2} across R₂ and R₃, and thereby allows Q₁ to conduct load current as V_{R2} approaches the base-to-emitter threshold of Q₁. The threshold (V_{BE}) is approximately 0.7V at room temperature.

Choose the values of R₁, R₂, and R₃ to ensure that R₂, R₃ and Q₁ dissipate maximum power at the maximum load current (320mA in this case). At 320mA, U1 conducts 200mA and Q1 conducts 120 mA. Component power dissipation at maximum load is as follows:

$$P_{R1} = I_{R1}^2 \times R_1 = 120\text{mA}^2 \times 9.1\Omega \approx 131\text{mW}$$

$$P_{Q1} = V_{Q1} \times I_{Q1} = (V_{SS} - V_{R1} - V_{OUT}) \times I_{Q1} = (5\text{V} - 1.1\text{V} - 2.5\text{V}) \times 120\text{mA} \approx 168\text{mW}$$

$$P_{R2} = I_{R2}^2 \times R_2 = 100\text{mA}^2 \times 18\Omega \approx 180\text{mW}$$

$$P_{R3} = I_{R3}^2 \times R_3 = 100\text{mA}^2 \times 18\Omega \approx 180\text{mW}$$

$$P_{U1} = V_{U1} \times I_{U1} = (V_{SS} - V_{R2} - V_{OUT}) \times I_{U1} = (5\text{V} - 1.8\text{V} - 2.5\text{V}) \times 200\text{mA} \approx 140\text{mW}$$

To provide higher load current, you can easily modify the circuit by increasing the power-dissipation ratings of R_1 , R_2 , R_3 , and Q_1 . **Table 1** details the components shown for 320mA load current. For power dissipation, the circuit board should have ample copper connected to the leads of power-dissipating components. Heat then conducts through the component leads to the circuit board, spreads into the copper areas, and is removed from the board by convection.

Table 1. Figure 1 Components

Component	Manufacturer Part Number Description	Package	Power Dissipation	Allowable Power Dissipation at +85°C
R_1	KAMAYA, INC. RMC18-9R1JB 9.1Ω ±5% Resistor	1206	250mW derate 4.55mW/°C above +70°C	181.75mW
R_2, R_3	KAMAYA, INC. RMC18-18RJB 18Ω ±5% Resistor	1206	250mW derate 4.55mW/°C above +70°C	181.75mW
Q_1	Central Semiconductor Corp. CMPT2222A NPN Transistor	SOT23-3	350mW derate 2.8mW/°C above +25°C	182mW
U_1	Maxim Integrated Products MAX1735EUK25 200mA Negative LDO	SOT23-5	571mW derate 7.1mW/°C above +70°C	464.5mW

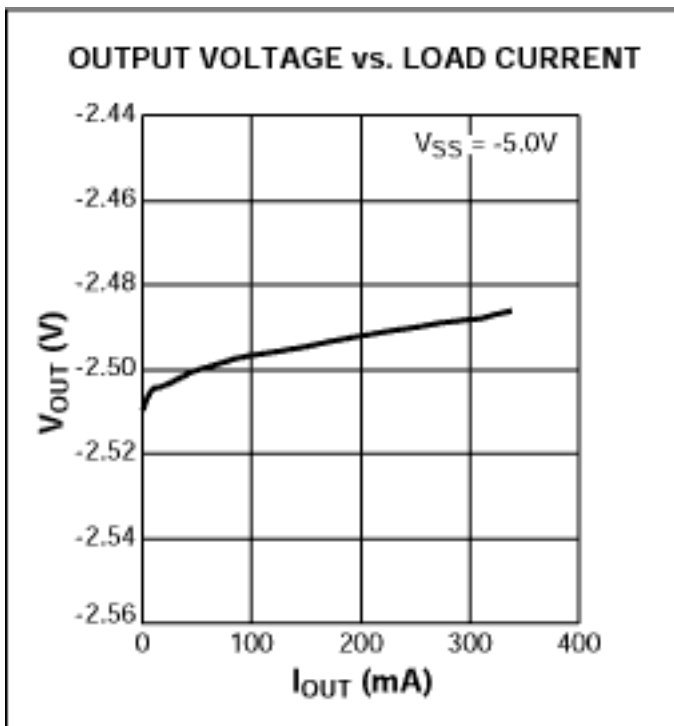


Figure 2a.

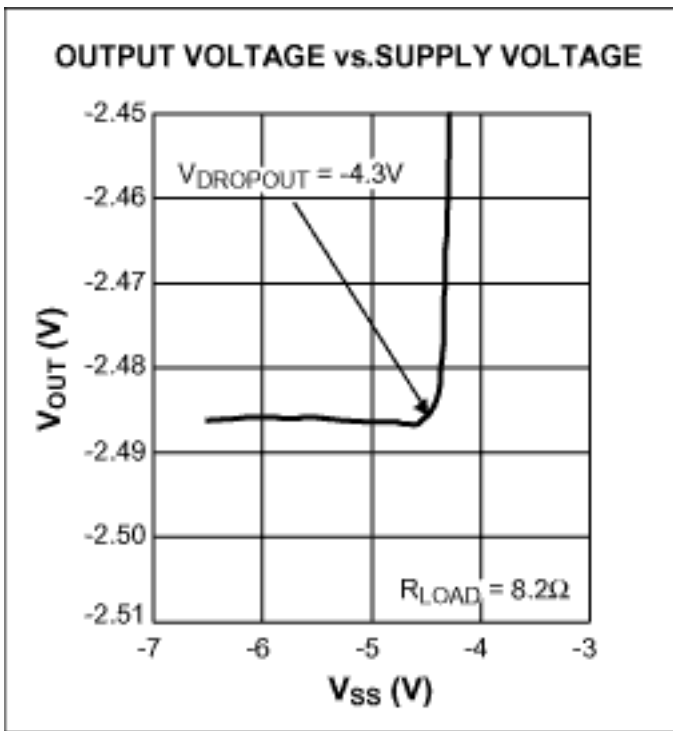


Figure 2b.

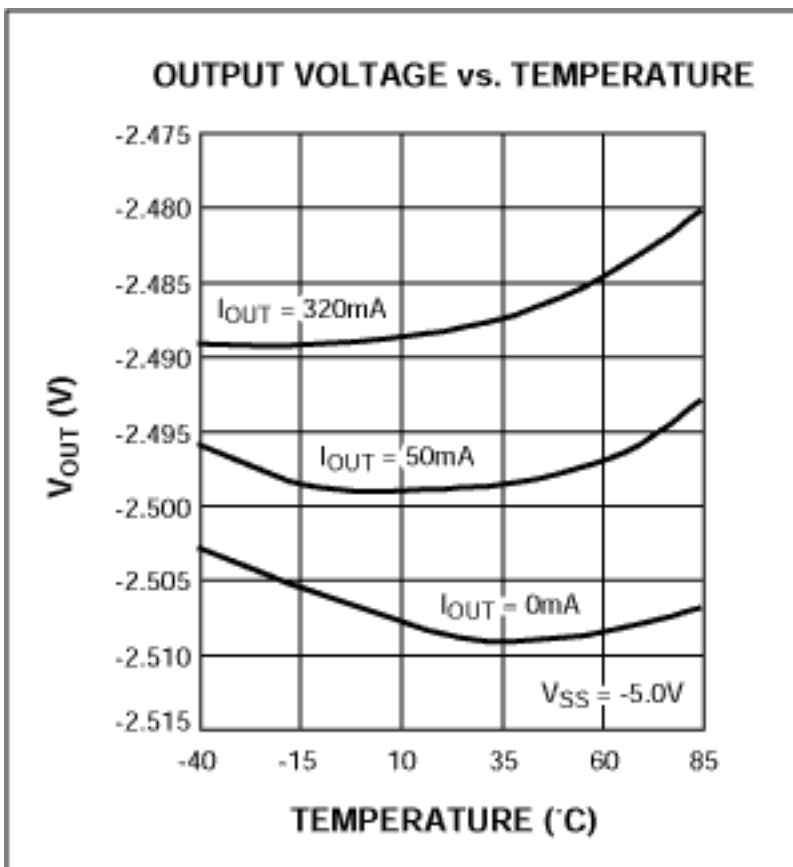


Figure 2c.

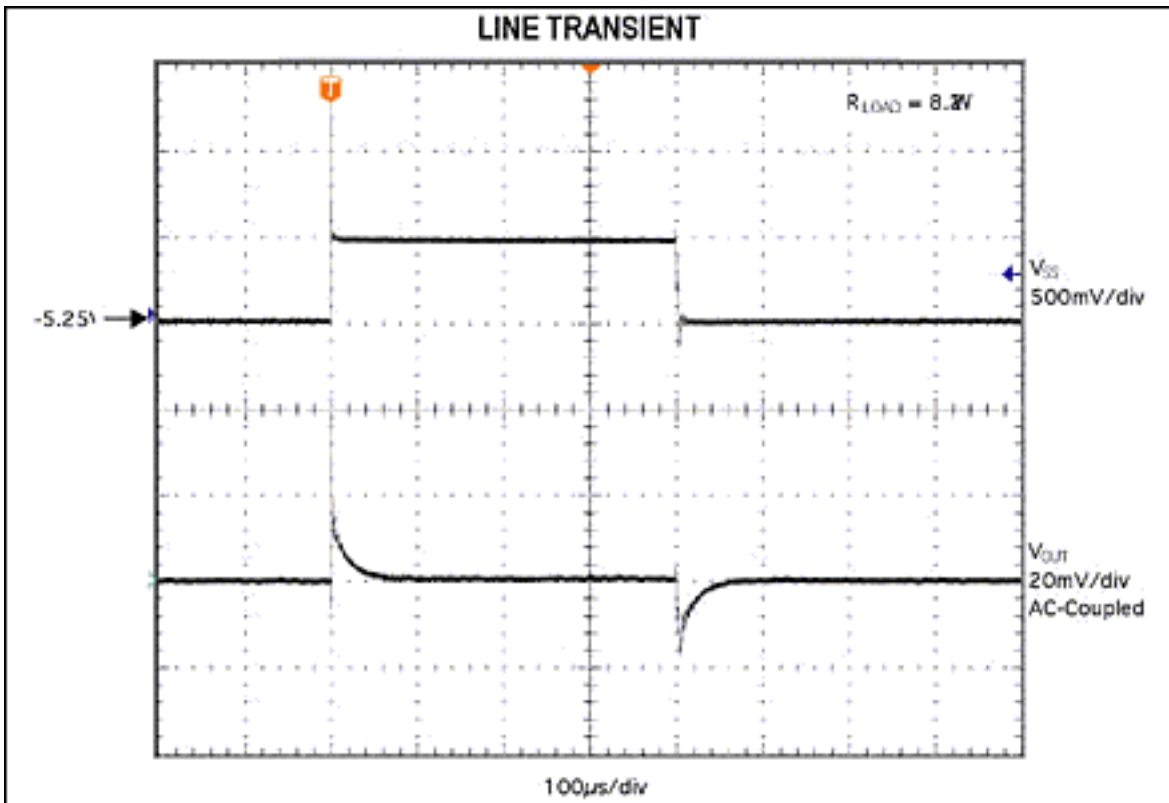


Figure 2d.

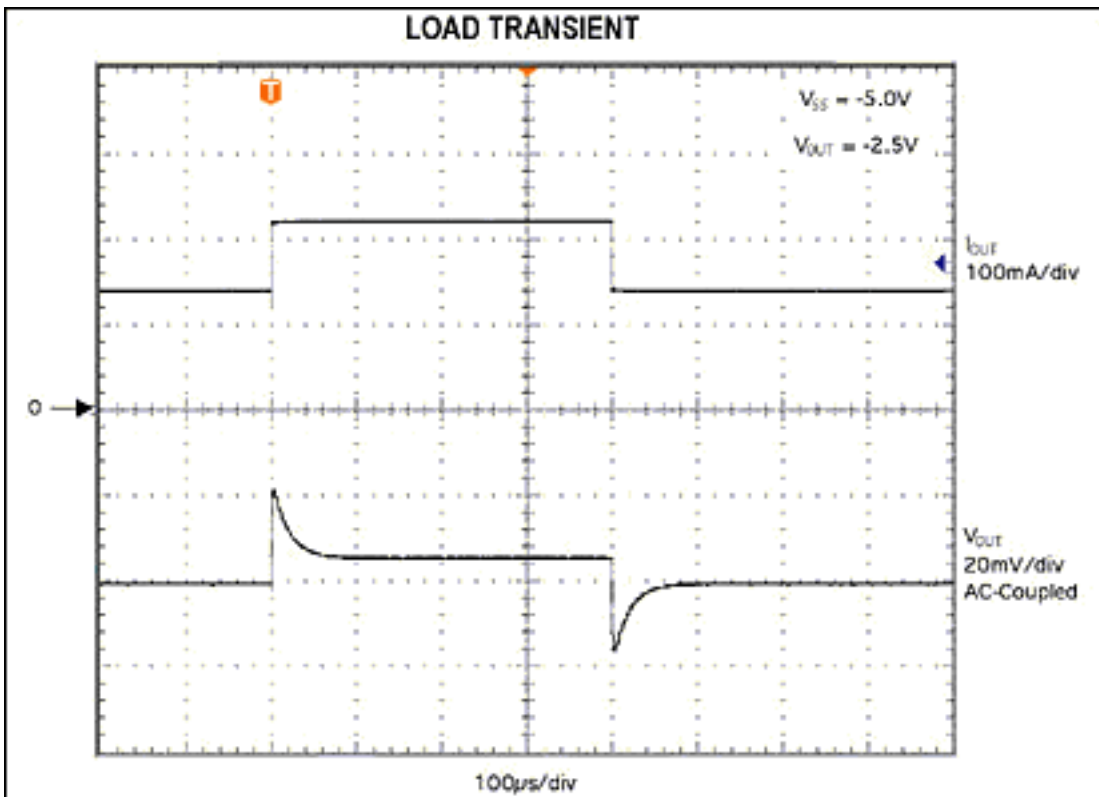


Figure 2e.

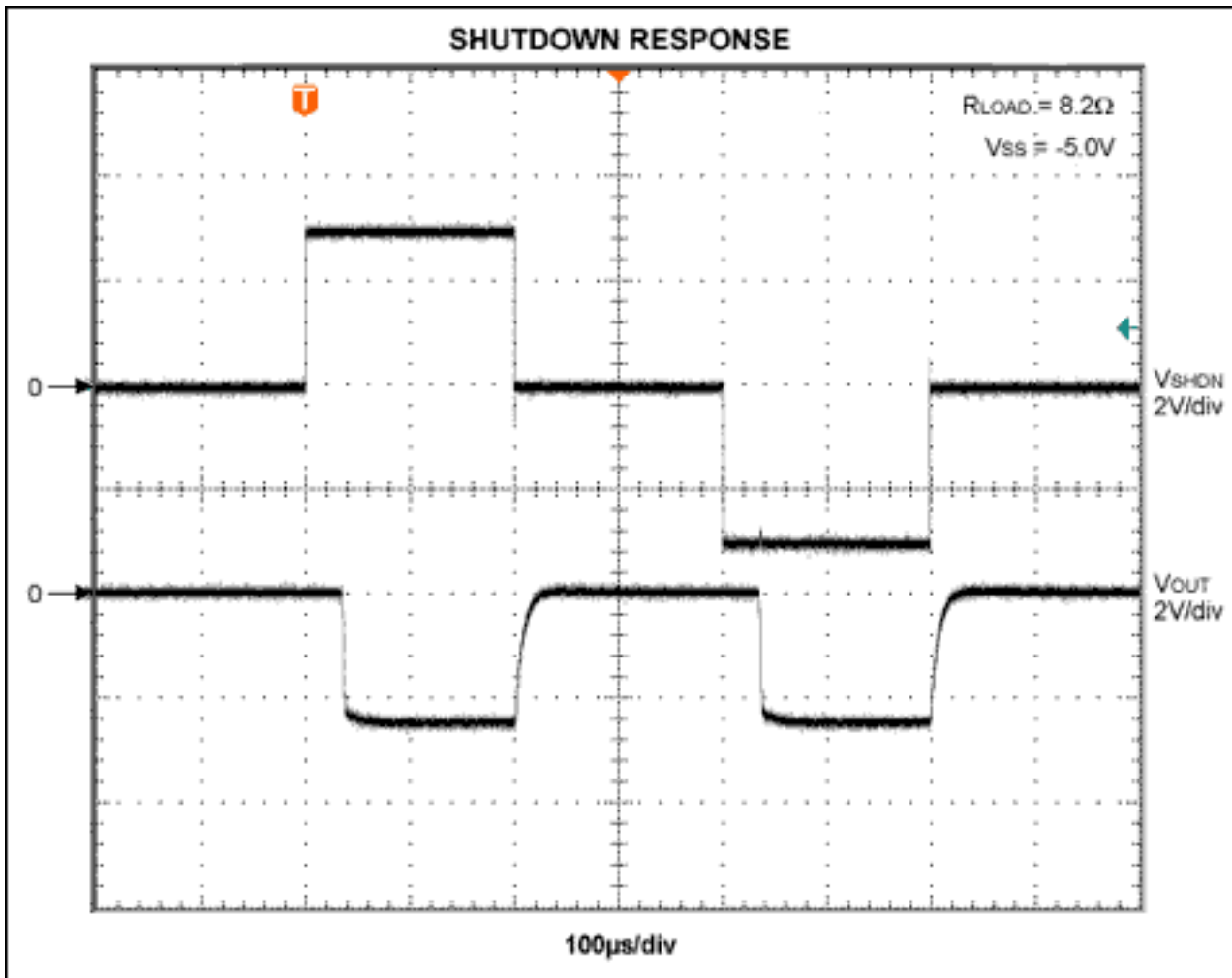


Figure 2f.

Figure 2. Curves and waveforms characterize the output of Figure 1: output voltage vs. load current (a), output voltage vs. supply voltage (b), output voltage vs. temperature (c), line transient response (d), load transient response (e), and shutdown response (f).

A similar version of this article appeared in the November 25, 2002 issue of *EDN* magazine.

Application Note 1861: www.maxim-ic.com/an1861

More Information

For technical questions and support: www.maxim-ic.com/support

For samples: www.maxim-ic.com/samples

Other questions and comments: www.maxim-ic.com/contact

Keep Me Informed

Preview new application notes in your areas of interest as soon as they are published. Subscribe to [EE-Mail - Application Notes](#) for weekly updates.

Related Parts

MAX1735: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN1861, AN 1861, APP1861, Appnote1861, Appnote 1861
Copyright © by Maxim Integrated Products
Additional legal notices: www.maxim-ic.com/legal