

APPLICATION NOTE 3305

Using the MAX4090 with the Reconstruction Filter

Abstract: In most video applications, the video signal generated from the DAC requires a reconstruction filter to smooth out the signal and attenuate the sampling aliases. The MAX4090 is a direct, DC-coupled output driver, which can be used after the reconstruction filter to drive the video signal. The driving load from the video DAC can be varied from 75Ω to 300Ω. A low input impedance (< 100Ω) is required by the MAX4090 in normal operation, special care must be taken when a reconstruction filter is used in front of the MAX4090.

For standard video signal, the video passband is about 6MHz and the system over-sampling frequency is at 27MHz. Normally, A 9MHz BW lowpass filter (LPF) is required for the reconstruction filter. The following paragraphs talk about the methods to build simple 2nd- and 3rd-order passive butterworth lowpass filters at 9MHz cutoff frequency and the techniques to use them with the [MAX4090](#) (**Figure 1** and **Figure 4**).

2nd-Order Butterworth Lowpass Filter Realization

Table 1 shows the normalized 2nd-order butterworth LPF component values at 1rad/s with a source/load impedance of 1Ω.

Table 1.

Rn1 = Rn2 (Ω)	Cn1 (F)	Ln1 (H)
1	1.414	1.414

With the following equations, the L and C can be calculated for the cutoff frequency at 9MHz. **Table 2** shows the appropriated L and C values for different source/load impedance and the bench measurement values for the -3dB BW and attenuation at 27MHz. There is approximately 20dB attenuation at 27MHz, which attenuates the sampling aliases effectively. The MAX4090 requires low input impedance for stable operation and it doesn't like the reactive input impedance. For R1/R2 greater than 100Ω, a series resistor R_{IS} (Figure 1) between 20Ω to 100Ω is needed to isolate the input capacitor (C4) to the filter to prevent the oscillation problem.

$$C = \frac{C_n}{2\pi f_c R_L} \quad L = \frac{L_n R_L}{2\pi f_c}$$

Table 2.

R1 = R2 (Ω)	C1 (pF)	L1 (μH)	R _{IS} (Ω)	3dB BW (MHz)	Attenuation at 27MHz (dB)
75	330	1.8	0	8.7	20
150	150	3.9	50	9	20
200	120	4.7	50	9.3	22
300	82	8.2	100	8.7	20

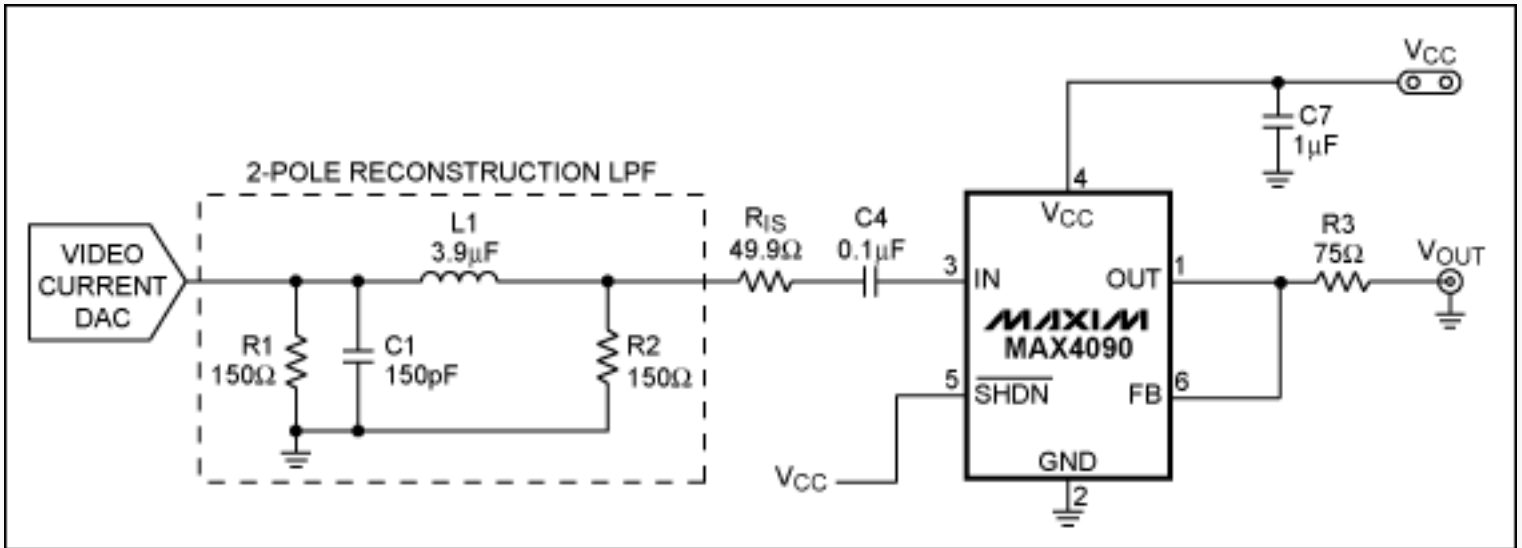


Figure 1.

Figure 2 shows the frequency response for $R1 = R2 = 150\Omega$. At 6MHz, the attenuation is about 1.4dB. The attenuation at 27MHz is about 20dB. **Figure 3** shows the multiburst response for $R1 = R2 = 150\Omega$.

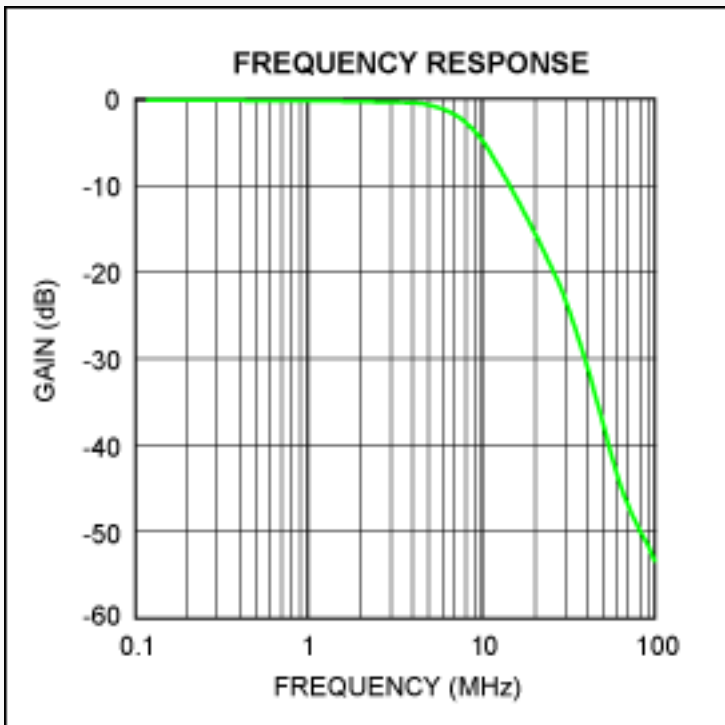


Figure 2. Frequency response.

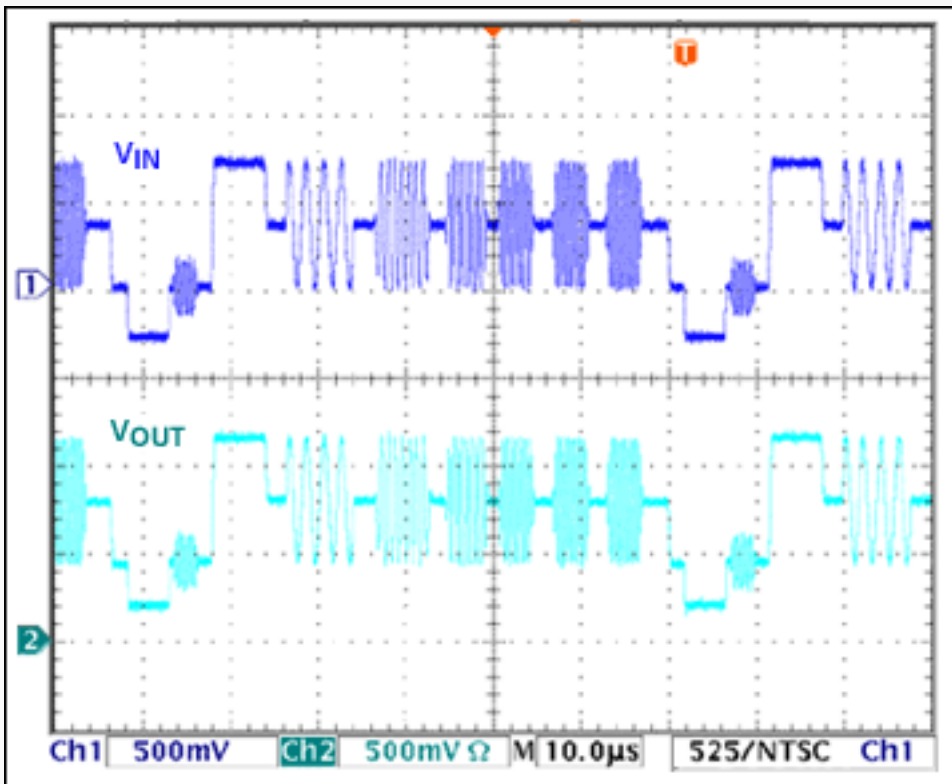


Figure 3. Multiburst response.

3rd-Order Butterworth Lowpass Filter Realization

If more flat passband and more stopband attenuation are needed, a 3rd-order LPF can be used.

Table 3 shows the normalized 3rd-order butterworth lowpass filter with the cut off frequency at 1rad/s and the stopband frequency at 3rad/s. **Table 4** shows the appropriated L and C values for different source/load impedance and the bench measurement values for -3dB BW and attenuation at 27MHz. The attenuation is over 40dB at 27MHz. At 6MHz, the attenuation is approximately 0.6dB for $R1 = R2 = 150\Omega$ (**Figure 5**).

Table 3.

$R_{n1} = R_{n2} (\Omega)$	$C_{n1} (F)$	$C_{n2} (F)$	$C_{n3} (F)$	$L_{n1} (H)$
1	0.923	0.923	0.06	1.846

Table 4.

$R1 = R2 (\Omega)$	$C1 (pF)$	$C2 (pF)$	$C3 (pF)$	$L (\mu H)$	$R_{IS} (\Omega)$	3dB BW (MHz)	Attenuation at 27MHz (dB)
75	220	220	15	2.2	0	9.3	43
150	120	120	6.8	4.7	50	8.9	50
300	56	56	3.3	10	100	9	45

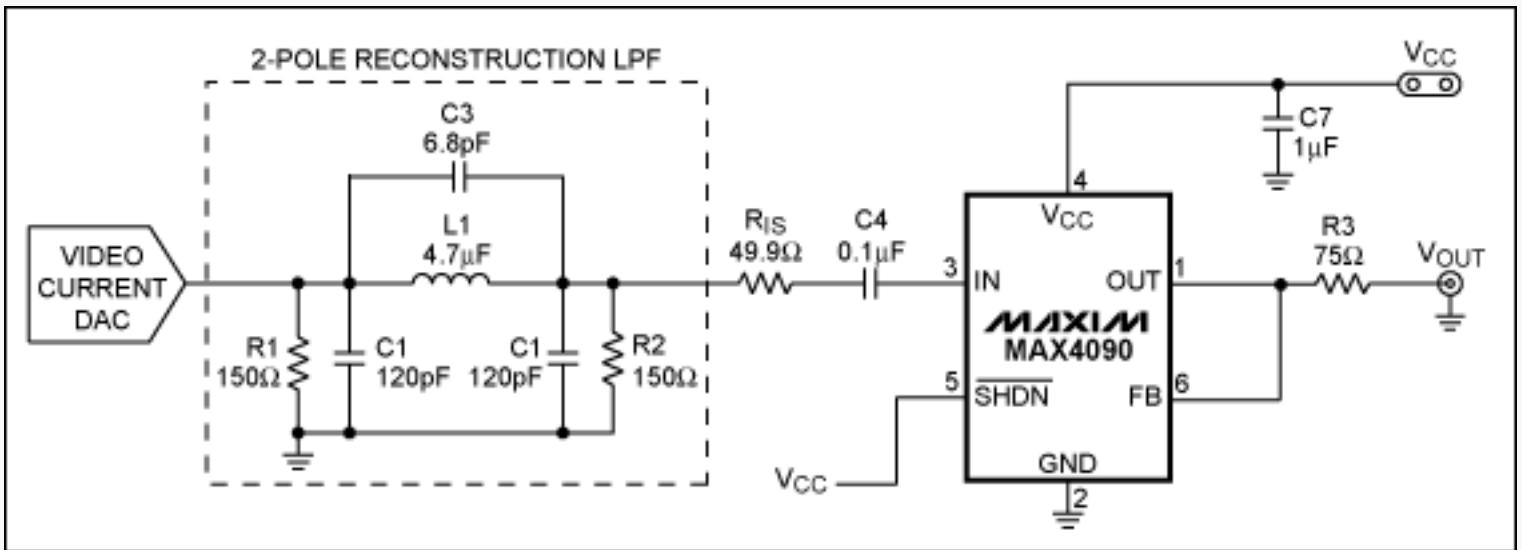


Figure 4.

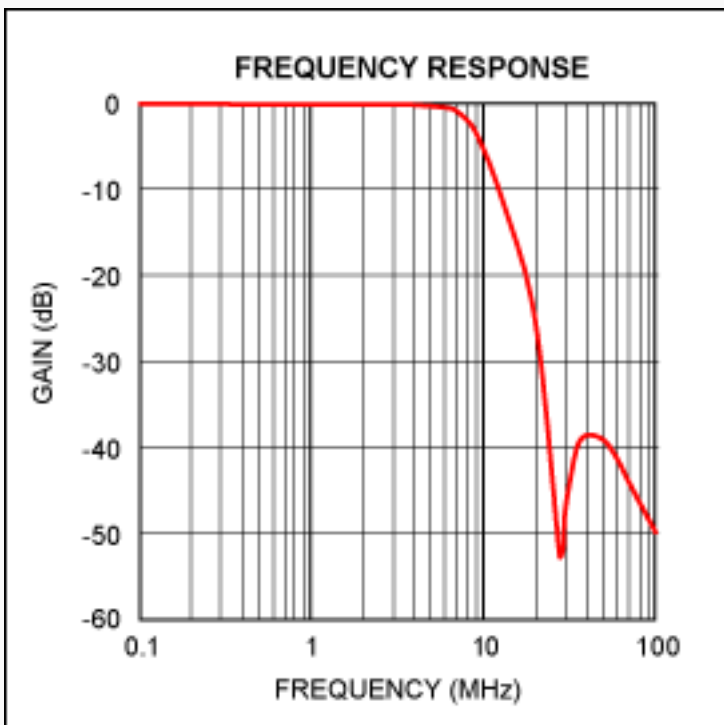


Figure 5.

Sag Correction

In a 5V application, the MAX4090 can use the Sag configuration if an AC-coupled output video signal is required. Sag correction refers to the low frequency compensation for the highpass filter formed by the 150Ω load and the output capacitor. In video application, the cutoff frequency must be low enough to pass the vertical Sync interval to avoid field tilt. This cutoff frequency should be less than 3Hz to 5Hz, and the coupling capacitor must be very large in normal configuration, typically > 220μF. In Sag configuration, the MAX4090 eliminates the need for large coupling capacitor, and instead requires two 22μF capacitors (**Figure 6**). Bench experiment shows that increasing the output coupling capacitor C5 beyond 47μF doesn't improve the performance. If the supply voltage is less than 4.5V, the Sag correction is not recommended for the MAX4090.

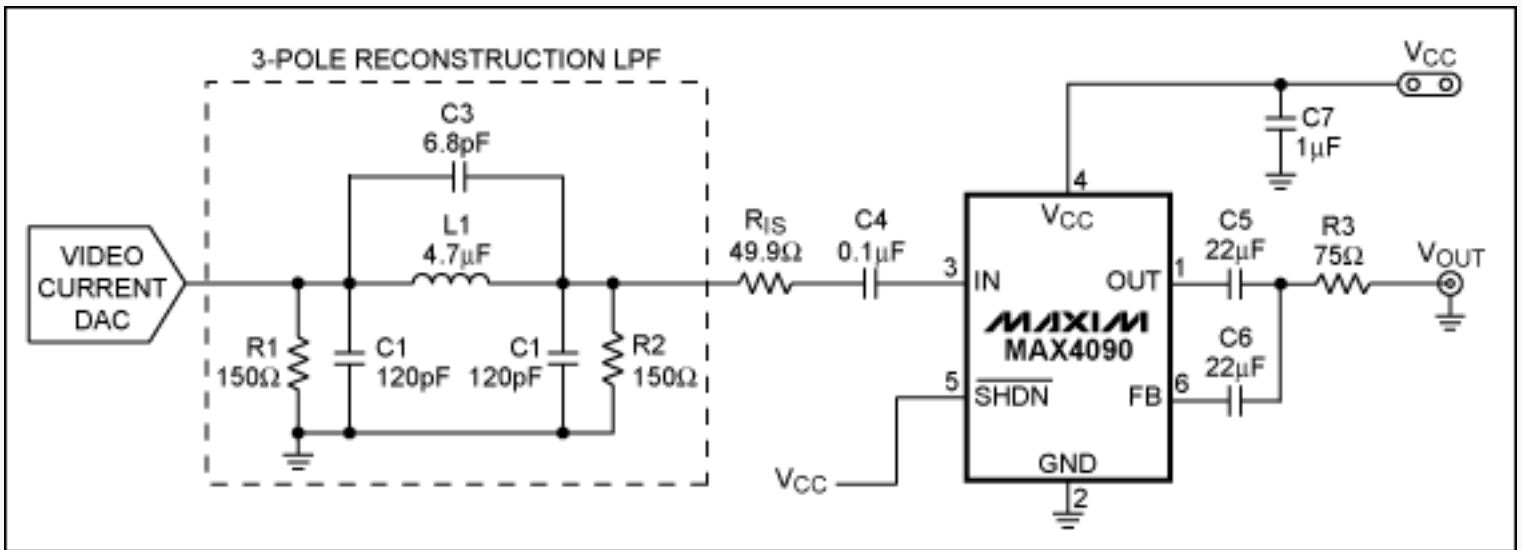


Figure 6.

Application note 3305: www.maxim-ic.com/an3305

More Information

For technical support: www.maxim-ic.com/support

For samples: www.maxim-ic.com/samples

Other questions and comments: www.maxim-ic.com/contact

Automatic Updates

Would you like to be automatically notified when new application notes are published in your areas of interest?

[Sign up for EE-Mail™.](#)

Related Parts

MAX4090: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN3305, AN 3305, APP3305, Appnote3305, Appnote 3305

Copyright © by Maxim Integrated Products

Additional legal notices: www.maxim-ic.com/legal