

APPLICATION NOTE 3872

# Telecomm Supply Powers Temperature Sensor

*Abstract: The components shown enable this temperature-to-period converter (IC1) to interface with standard industrial logic levels, while operating on a -48V telecomm systems bus. The circuit presented features the MAX6576 digital temperature sensor.*

Integrated-circuit temperature sensors are generally preferred in data-acquisition systems for which the accuracy demands are not extreme. Sensor, signal-processing, and data-conversion electronics, plus an easy-to-use digital-I/O interface are all integrated in the temperature sensor IC, and all at low cost. Such ICs require a supply voltage in the range +3V to +5V, negative to common, and they usually draw very low supply current.

Biasing the sensor is more difficult in a telecomm system, however, where the only supply voltage available is usually the -48V systems bus. If no other positive low-voltage supply is available, the design must normally include a DC-DC converter powered from -48V.

The circuit of **Figure 1** solves the above problem without needing an extra power supply. This circuit allows the IC sensor to operate from -48V. With the addition of a few components, it also serves as an interface to the digital inputs of programmable-logic controllers (PLCs) or other digital I/O that require logic signals ranging from 0V to some positive level. As shown here, the output can sink up to 1.6mA, and swing from 0V to about +40V (the maximum  $V_{CE}$  for a 2N3904 transistor). That capability meets the requirements for digital I/O in most industrial systems (+15 or +5V).

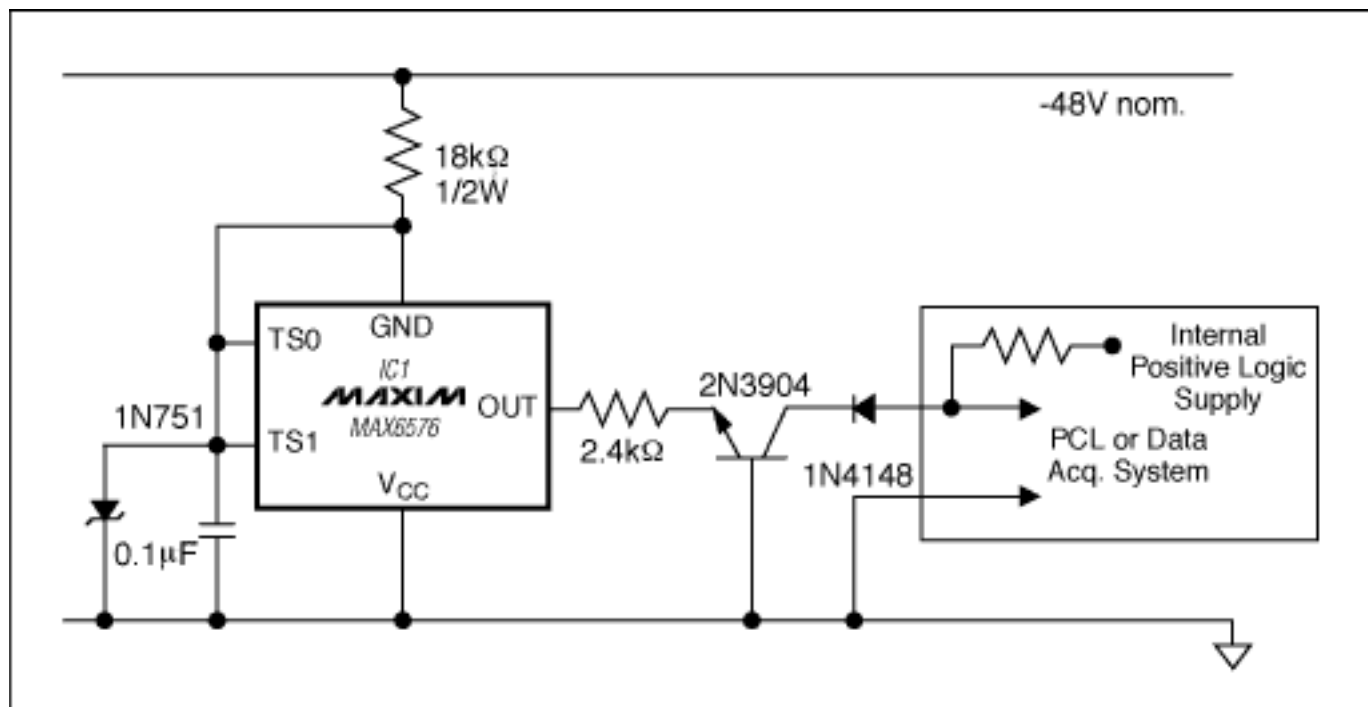


Figure 1. The components shown enable this temperature-to-period converter (IC1) to interface with standard industrial logic levels while operating on a -48V telecomm systems bus.

The circuit in Figure 1 includes an absolute temperature-to-period converter (IC1). Connected as shown, it provides a conversion constant of  $640\mu s/^{\circ}K$ . (At room temperature the period is about 190ms, giving a

frequency of 5.2Hz.) This scheme can also accommodate similar sensors, such as temperature-to-frequency converters. For a listing of accuracy specifications and other parameters associated with IC1, please see the [MAX6576 data sheet](#).

This design idea appeared in the February 16, 2006 issue of *ED*.

---

Application Note 3872: <http://www.maxim-ic.com/an3872>

### **More Information**

For technical questions and support: <http://www.maxim-ic.com/support>

For samples: <http://www.maxim-ic.com/samples>

Other questions and comments: <http://www.maxim-ic.com/contact>

### **Related Parts**

MAX6576: [QuickView](#) -- [Full \(PDF\) Data Sheet](#)

AN3872, AN 3872, APP3872, Appnote3872, Appnote 3872

Copyright © by Maxim Integrated Products

Additional legal notices: <http://www.maxim-ic.com/legal>