



APPLICATION NOTE 4255

# How to Power the Extended Features of 1-Wire® Devices

*Abstract: A 1-Wire bus provides both communication and power between a host and slave devices on a single line. Some 1-Wire devices offer extended features, which include EEPROM, temperature measurement, and a SHA-1 engine. Operation of these special features can require additional power, so the 1-Wire device's pull-up resistor ( $R_{PUP}$ ) must be sized accordingly.*

## Introduction

The 1-Wire bus is a simple signaling scheme that performs half-duplex bidirectional communications between a master controller and one or more slaves, all sharing a common data line. Both power delivery and data communication take place over this single line. Most 1-Wire devices use very little power, on the order of tens of microamps, to operate and communicate. Some 1-Wire devices, however, need more power during specific operations, such as an EEPROM write or a device-specific calculation or measurement. During these periods of increased power demand, it is important that the voltage on the 1-Wire bus does not fall below the device's minimum operating pullup voltage ( $V_{PUP}$ ). For most parasitic-powered 1-Wire devices, the minimum operating voltage ( $V_{PUP}$ ) is 2.8V.

## 1-Wire Devices that Need Extra Power

Table 1 is a partial list of 1-Wire devices with special features that require extra power.

Table 1. Devices that Need Extra Power

Part	EEPROM	SHA-1	Temperature	ADC
DS18B20	✓		✓	
DS1920	✓		✓	
DS1961S	✓	✓		
DS1971	✓			
DS1972	✓			
DS1973	✓			
DS1977	✓			
DS2431	✓			
DS2432	✓	✓		
DS2433	✓			
DS2450				✓
DS28E01-100	✓	✓		
DS28E04-100	✓			
DS28EA00	✓		✓	
DS28EC20	✓			

## How to Identify Extra Power Requirements in the EC Table

Any additional power requirements for a device are listed in the data sheet's electrical characteristics (EC) table under a variety of terms (**Table 2**). The pullup resistor's specification ( $R_{PUP}$ ) in the EC table is for 1-Wire communication only and does not include additional power requirements for the special operations.

**Table 2. EC Table Parameters Specifying Extra Power Demands**

Parameter Description	Symbol	1-Wire Device
Programming Current	$I_{PROG}$	DS1961S, DS1972, DS2431, DS28E01, DS28E04, DS28E00
Programming Current	$I_{LPROG}$	DS1973, DS2433, DS1977, DS2432
Programming Current	$I_P$	DS1971 (DS2430A)
SHA Computation Current	$I_{LCSHA}$	DS1961S, DS28E01
Active Current	$I_{DD}, I_{DQA}$	DS1920, DS18B20, DS18B20-PAR
Conversion Current	$I_{CONV}$	DS28EA00
Operating Current	$I_{CC}$	DS2450

Parameter	Symbol	Conditions	Min	Typ	Max	Units
<b>EEPROM</b>						
Programming Current	$I_{PROG}$	(Notes 5, 20)			1.5	mA
Programming Time	$t_{PROG}$	(Note 21)			10	ms
Write/Erase Cycles (Endurance) (Notes 22, 23)	$N_{CY}$	At +25°C	200k			—
		-40°C to +85°C	50k			
Data Retention (Notes 24, 25)	$t_{DR}$	At +85°C (worst case)	10			years
<b>Temperature Converter</b>						
Conversion Current	$I_{CONV}$	(Notes 5, 20)			1.5	mA

Figure 1. Example of the EC table for the [DS28EA00](#).

### Available Power

For a given  $V_{PUP}$  and  $R_{PUP}$ , the voltage difference between  $V_{PUP}$  and the 1-Wire device's  $V_{PUPmin}$  determines the current available for special functions. The available current can be calculated as  $I_{AVAIL} = (V_{PUP} - V_{PUPmin})/R_{PUP}$ . An example calculation follows:

$$V_{PUP} = 5V$$

$$R_{PUP} = 2k\Omega$$

$$V_{PUPmin} = 2.8V, \text{ resulting in } I_{AVAIL} = 1.1mA$$

So for this example, there are 1.1mA available before the 1-Wire voltage drops below the minimum  $V_{PUP}$ . If the available current is not sufficient for the application, then a lower pullup resistor or a low-impedance bypass to the pullup resistor will be necessary.

### Finding the Right Pullup ( $R_{PUP}$ )

The available current can be calculated by dividing the potential voltage drop from nominal  $V_{PUP}$  to the minimum  $V_{PUP}$  by the pullup resistor ( $R_{PUP}$ ). **Figure 2** graphs this calculation based on a  $V_{PUP}$  of 5V with a device that has a minimum  $V_{PUP}$  of 2.8V. A pullup resistor of 2.2k $\Omega$  or less supports at least 1mA at 5V pullup voltage.

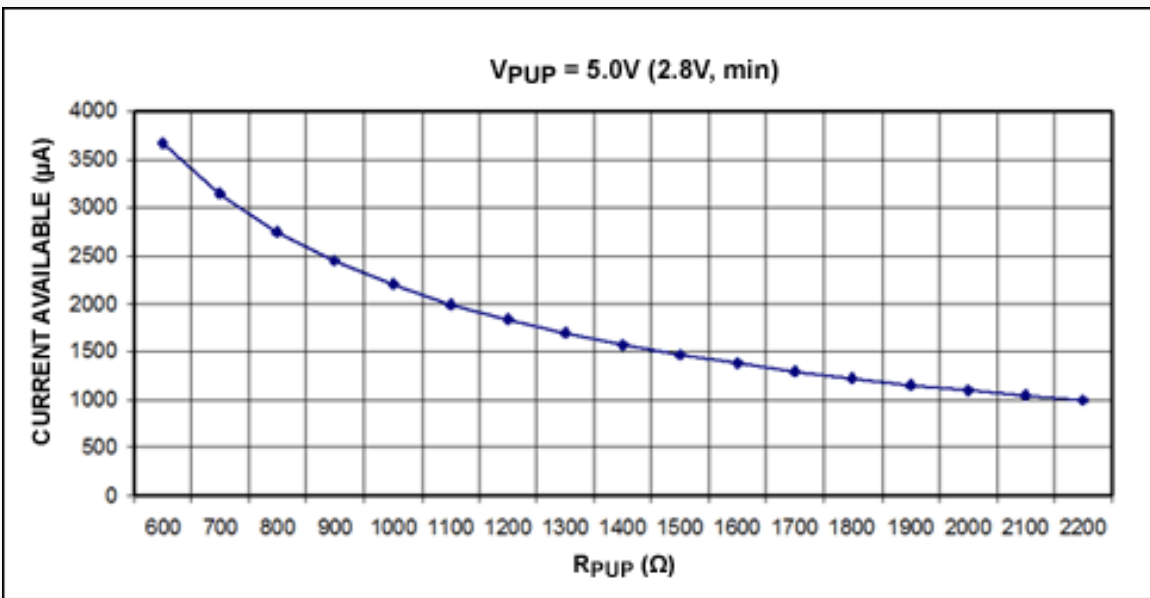


Figure 2. Available current for  $V_{pUP} = 5V$ .

Similarly, **Figure 3** shows the available current based on a  $V_{pUP}$  of 3.3V. With only 0.5V as the permissible voltage drop on the pullup resistor, very little current is available. Other means of providing the extra current are probably required (see **Low-Impedance Bypass** section below).

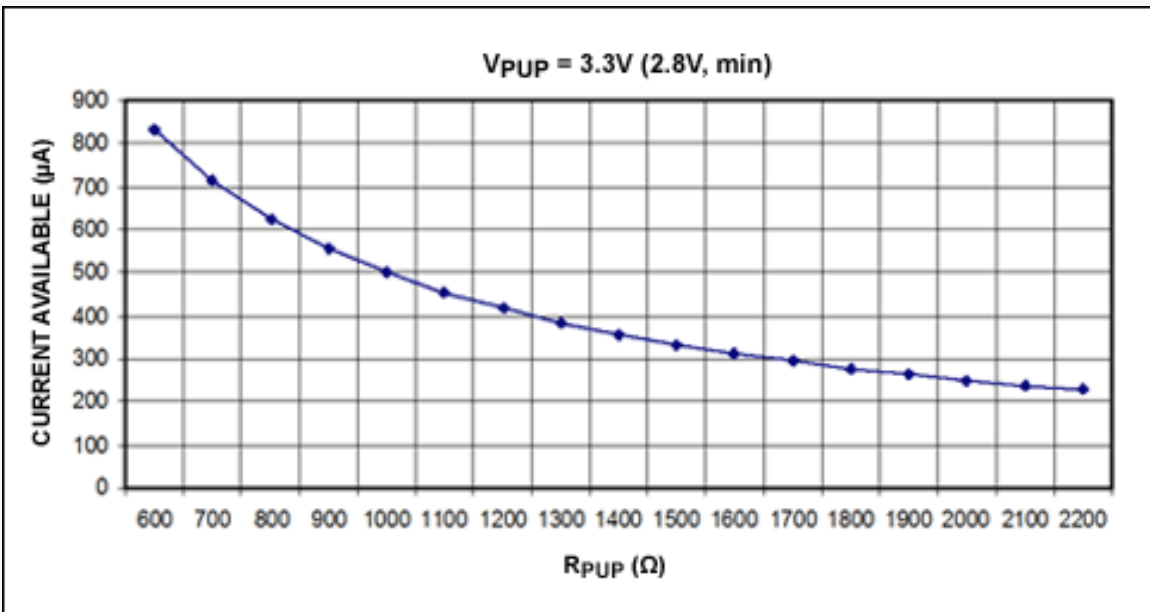


Figure 3. Available current for  $V_{pUP} = 3.3V$ .

### Advanced Considerations

Choosing a very-low pullup resistor value delivers the desired power to run the special function. However, this configuration raises the voltage representing logic 0 on the 1-Wire bus. If  $V_{OL}$  levels do not meet the minimum-voltage input low ( $V_{IL}$ ) specified for the 1-Wire slave or the 1-Wire master, then reliable communication will not be possible. The most common  $V_{OL}$  specification for 1-Wire devices is 0.4V at 4mA, maximum. This value is equivalent to an impedance of 100 $\Omega$ , maximum, when the 1-Wire device is responding with a logic 0.  $V_{IL}$  varies from 0.3V to 0.8V, depending on the 1-Wire device. With multiple 1-Wire devices on the bus, the lowest  $V_{IL}$  sets the limit. The pullup resistor value that meets the logic 0 requirement can be calculated as:  $R_{pUPmin} = 100\Omega \times (V_{pUP}/V_{ILmax} - 1)$ .

(**Note:** Instead of starting the equation with 100 $\Omega$ , one could write  $V_{OL}/4mA$ .)

Therefore, assuming a  $V_{IL}$  maximum of 0.4V, the results are

For a  $V_{PUP} = 5V$ :  $1150\Omega$

For  $V_{PUP} = 3.3V$ :  $725\Omega$

Assuming a  $V_{IL}$  maximum of  $0.3V$ , the results are

For a  $V_{PUP} = 5V$ :  $1567\Omega$

For  $V_{PUP} = 3.3V$ :  $1000\Omega$

The tolerances for the pullup resistor and the power supply must also be considered when selecting the proper pullup. These tolerances are not correlated, i.e., they can add up to either (positive, negative) side or cancel each other. Always check the worst combinations: voltage at upper limit with resistor at lower limit (i.e., highest  $V_{OL}$ ), and voltage lower limit with resistor at upper limit (i.e., lowest available extra current).

## Low-Impedance Bypass

If meeting the  $V_{OL}$  and  $V_{IL}$  requirements requires a pullup resistor that cannot deliver the necessary current, then the extra current must be supplied by other means. There are two ways to do this:

1. Implement a discrete low impedance bypass (also called a strong pullup) that is engaged only during high current demand.
2. Utilize a 1-Wire interface device that incorporates a strong pullup.

Examples of a 1-Wire master with a discrete strong pullup can be found in application note 4206, "[Choosing the Right 1-Wire® Master for Embedded Applications](#)," or application note 244, "[Advanced 1-Wire Network Driver](#)." **Figure 4** shows a strong pullup controlled with an extra IO pin.

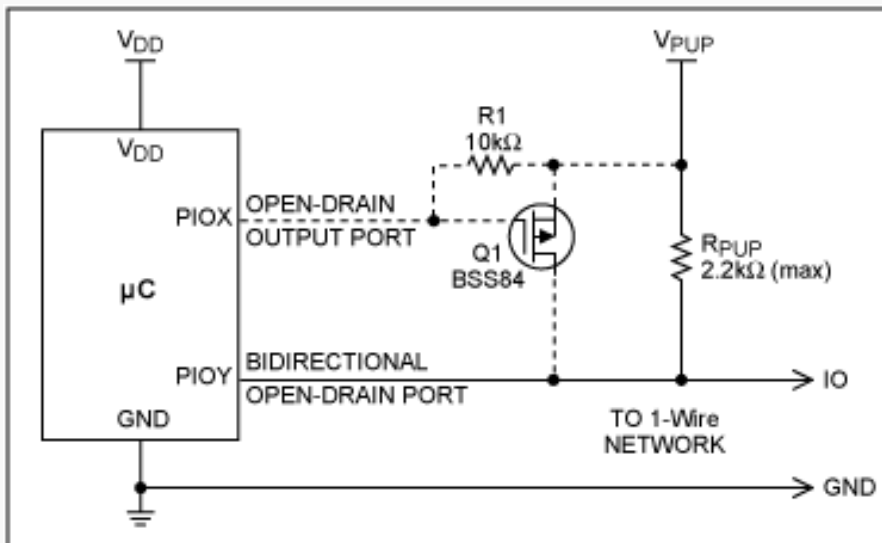


Figure 4. Bidirectional port pin with optional circuit for strong pullup (dashed lines).

There are three 1-Wire interface chips that incorporate a strong pullup feature (**Table 3**). The DS2482-100 also has an external control signal that can be used to drive an additional discrete, extra-strong pullup.

**Table 3. 1-Wire Master Interface Devices**

Device	Interface	Features
DS2480B	Serial	Strong pullup, active pullup
DS2482-100	I <sup>2</sup> C	Single 1-Wire channel with built in strong pullup, optional active pullup, control signal for extra-strong pullup
DS2482-800	I <sup>2</sup> C	Eight 1-Wire channels with built in strong pullup, optional active pullup

## Conclusion

For extended features like temperature conversion, EEPROM, or a SHA-1 engine to operate properly in 1-Wire devices, those devices must be provided with sufficient current from the 1-Wire master without allowing the 1-Wire to drop below the minimum-voltage pullup ( $V_{PUP}$ ). The 1-Wire pullup resistor ( $R_{PUP}$ ) must, therefore, be sized to provide this current in accordance with application demands. If application requirements do not permit a pullup resistor of the correct size, then the current can be supplied with a discrete strong pullup circuit or a 1-Wire interface chip such as the DS2480B or DS2482.

1-Wire is a registered trademark of Maxim Integrated Products, Inc.

---

Application note 4255: [www.maxim-ic.com/an4255](http://www.maxim-ic.com/an4255)

### More Information

For technical support: [www.maxim-ic.com/support](http://www.maxim-ic.com/support)

For samples: [www.maxim-ic.com/samples](http://www.maxim-ic.com/samples)

Other questions and comments: [www.maxim-ic.com/contact](http://www.maxim-ic.com/contact)

---

### Automatic Updates

Would you like to be automatically notified when new application notes are published in your areas of interest? [Sign up for EE-Mail™](#).

---

### Related Parts

DS18B20: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

DS1920: [QuickView](#) -- [Full \(PDF\) Data Sheet](#)

DS1961S: [QuickView](#)

DS1971: [QuickView](#) -- [Full \(PDF\) Data Sheet](#)

DS1972: [QuickView](#) -- [Full \(PDF\) Data Sheet](#)

DS1973: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

DS1977: [QuickView](#) -- [Full \(PDF\) Data Sheet](#)

DS2431: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

DS2432: [QuickView](#) -- [Abridged Data Sheet](#)

DS2433: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

DS2450: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

DS28E01-100: [QuickView](#) -- [Abridged Data Sheet](#)

DS28E04-100: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

DS28EA00: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

DS28EC20: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN4255, AN 4255, APP4255, Appnote4255, Appnote 4255

Copyright © by Maxim Integrated Products

Additional legal notices: [www.maxim-ic.com/legal](http://www.maxim-ic.com/legal)