

Keywords: pulse-frequency modulation, PFM, pulse-width modulation, PWM, low-current, isolated dc-dc supply, dc-dc converter, discontinuous operation, standby, green, idle current, PFM controller

Mar 19, 2009

#### APPLICATION NOTE 4326

## Reduce Standby Power Drains with Ultra-Low-Current, Pulse-Frequency-Modulated (PFM) DC-DC Converters

By: Javier Monsalve Kägi, Senior Member of Technical Staff, Applications  
Jose Miguel de Diego, Escuela Técnica Superior de Ingeniería, Bilbao, Spain  
Jose Ignacio Garate, Escuela Técnica Superior de Ingeniería, Bilbao, Spain

*Abstract: This article explains how to reduce the level of low-current consumption in isolated DC-DC power supplies and how to improve the performance of those supplies under no-load conditions. Sensitive to today's need for innovative "green" solutions, the discussion especially focuses on ways to extend the battery life of battery-powered electronic devices and communication-system devices with discontinuous transmission.*

This article was also featured in [Maxim's Engineering Journal](#), vol. 65 (PDF, 756kB).

A Japanese version of this article appeared in the *EDN Japan Power Supplement*, December, 2008.

Today, many industrial systems employ battery-powered sensors and transponders to eliminate expensive cable installations and to reduce overall system power consumption. These industrial systems typically have an active mode and a standby mode. In active mode the sensor delivers data to the transponder (a radio modem) which transmits the data to a host system. In standby mode the transponder and sensor go to sleep for a fixed or variable time period. This start-and-stop operation, often referred to as a discontinuous operating mode, maximizes the battery life of the device.

For an application like a watering system that leverages GSM radio modules for the sensors, maintenance costs would be high if the batteries powering the GSM radios had to be replaced every few days, or even every few weeks. Since such a system spends most of its time in standby or sleep mode, minimizing the power drain from the battery when no activity is taking place would go a long way toward extending battery life. In this system no-load quiescent current becomes a key design consideration, and for safety concerns, galvanic isolation is an important aspect of the design.

To address these concerns, designers must focus on the design of the DC-DC converter to ensure that it consumes as little current as possible during no-load conditions. All DC-DC converters, even during standby, can consume significant quiescent current. One commercial power-supply module (the RECOM® R-78A3.3-1OR), for example, draws about 7mA under no-load conditions. However, with some attention to topology and careful design, an isolated DC-DC converter module with a no-load current drain of less than 1mA can be implemented.

The 30x difference in current drain can translate into reduced battery replacements. For example, even if the system's batteries are rechargeable, then additional recharge cycles might be needed if the higher current-drain supply is used. Moreover, batteries that are recharged often, wear out sooner and end up in landfills. Similarly, if the device employs one-time-use batteries, they will discharge sooner with a higher standby current and get discarded more frequently.

While there are several approaches to the challenge, this article looks at the use of pulse-frequency modulation (PFM) to achieve a 1700:1 ratio between the device's on and standby states.

### System Characteristics

Typical power consumption versus time looks like the graph in **Figure 1**. Here the load current spikes during operation or active charging, and then drops when the device is idle. The idle current,  $I_z$ , must be minimized to reduce battery drain and extend battery life and standby time. Thus, the isolated DC-DC converter needs ultra-low-current consumption when no load is connected, and should also provide high isolation from input to output. Ideally, the converter should also offer high-conversion efficiency and a small footprint.

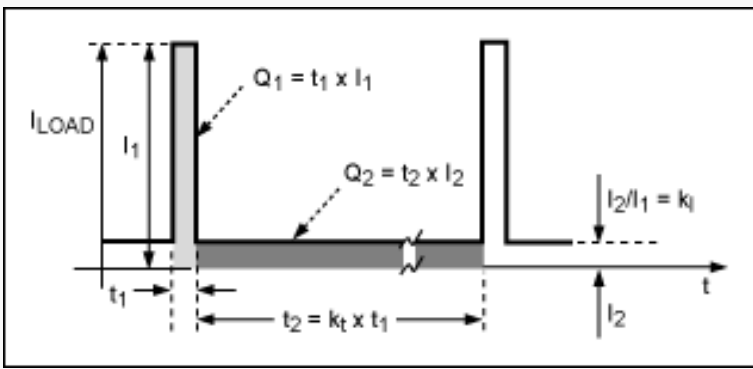


Figure 1. The relationship between the on and standby states of a communication device with discontinuous transmission.

The typical commercial DC-DC converters listed in **Table 1** show input currents of 7mA to 40mA when no load is connected with an input of 12V. These converters traditionally employ pulse-width-modulation (PWM) controllers. However, PWM controllers always have an active oscillator, even when there is no load, and that oscillator continually draws current from the battery.

**Table 1. Characteristics of Commercial DC-DC Converters**

Manufacturer	Model	V <sub>IN</sub> (V)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	I <sub>IN</sub> (I <sub>OUT</sub> = 0, mA)	η (%)	Isolation
Traco® Electronic AG	TEN 5-1210	12	3.3	1.2	20	77	✓
XP Power	JCA0412S03	12	3.3	1.2	38	83	✓
RECOM International Power	RW-123.3S	12	3.3	0.7	21	65	✓
C&D Technologies®	HL02R12S05	12	5	0.4	40	60	✓
Bourns® Inc.	MX3A-12SA	12	3.3	3.0	11	93	
RECOM International Power	R-78A3.3-1	12	3.3	1.0	7	81	

## A PFM Controller Topology

An alternative approach is to use a DC-DC converter that employs a pulse-frequency-modulation (PFM) controller.<sup>1</sup> A PFM controller uses two one-shot circuits that only work when the load drains current from the DC-DC converter's output. The PFM is based on two switching times (the maximum on-time and the minimum off-time) and two control loops (a voltage-regulation loop and a maximum peak-current, off-time loop).

The PFM is also characterized by control pulses of variable frequency. The two one-shot circuits in the controller define the T<sub>ON</sub> (maximum on-time) and the T<sub>OFF</sub> (minimum off-time). The T<sub>ON</sub> one-shot circuit activates the second one-shot, T<sub>OFF</sub>. Whenever the comparator of the voltage loop detects that V<sub>OUT</sub> is out of regulation, the T<sub>ON</sub> one-shot circuit is activated. The time of the pulse is fixed up to a maximum value. This pulse time can be reduced if the maximum peak-current loop detects that the current limit is surpassed.

The quiescent current consumption of a PFM controller is limited only to the current needed to bias its reference and error comparator (10s of μA). In contrast, the internal oscillator of a PWM controller must be turned on continuously, leading to a current consumption of several milliamps. The implementation presented in this article keeps the current consumption to less than 1mA at 12V by using a PFM controller topology.

Field systems such as the watering system must endure harsh environments, and thus the DC-DC converter in those systems should be galvanically isolated. A transformer provides the isolation, but the challenge is to feed back the voltage reference from the secondary side to the primary side without breaking the isolation. The most common approach solves the problem by using either an auxiliary winding or an optocoupler.

The power-supply topology is a step-down approach; the battery pack used by the application has a nominal voltage of 12V, while the internal electronic circuits in the system operate at 3.6V, nominal. **Figure 2** shows the schematic diagram of the DC-DC switching regulator and the bill of materials with component values is provided in **Table 2**. When the control loop is regulating the voltage, the optocoupler requires a constant current through the LED on the primary side of the transformer. The lower limit of the current is fixed by the optocoupler's CTR at low bias currents (63% at 10mA, and 22% at 1mA) and by a reduction of the response time (2μs at 20mA and 6.6μs at 5mA).




## Controlling It All

To implement a PFM controller, the MAX1771 BiCMOS step-up, switch-mode power-supply controller (U1) can be used to provide the necessary timing. The MAX1771 offers improvements over prior pulse-skipping control solutions: reduced size of the inductors required, due to a 300kHz switching frequency; the current-limited PFM control scheme achieves 90% efficiencies over a wide range of load currents; and a maximum supply current of just 110 $\mu$ A. Besides these advantages, the main characteristics of the MAX1771 in a nonisolated application are: 90% efficiency with load currents ranging from 30mA to 2A; up to 24W of output power; and an input-voltage range of 2V to 16.5V.

The resistances of the voltage-control loop have been chosen to have the highest possible values. This decision represents a trade-off between current consumption and loop stability. As a result, the current through the voltage-divider is less than 7 $\mu$ A. Since the filtering capacitors are nonideal, capacitor leakage current must be added to this current. In this design, filter capacitor-leakage current in C5 and C8 is less than 20 $\mu$ A. If lower leakage is required, these caps could be upgraded to ceramic capacitors with the following characteristics: 100 $\mu$ F, 6.3V, X5R, and 1206 size (Kemet C1206C107M9PAC). Using ceramic capacitors reduces the capacitor leakage to just a few microamps. Note, however, that the ceramic capacitors cost about 3x that of the tantalum capacitors, and that difference would increase the system cost.

**Figure 3** shows the prototype PFM DC-DC converter that draws a quiescent current of just 0.24mA. The board measures less than 50mm by 30mm, can deliver 3.6W with an input-voltage range of 10V to 15V (12V nominal), and operates at a switching frequency of 300kHz. The converter can supply a maximum constant output current of 1A while delivering a regulated output of 3.6V. Employing a flyback topology (step down) with both current and voltage feedback control, the converter output is galvanically isolated from the input.

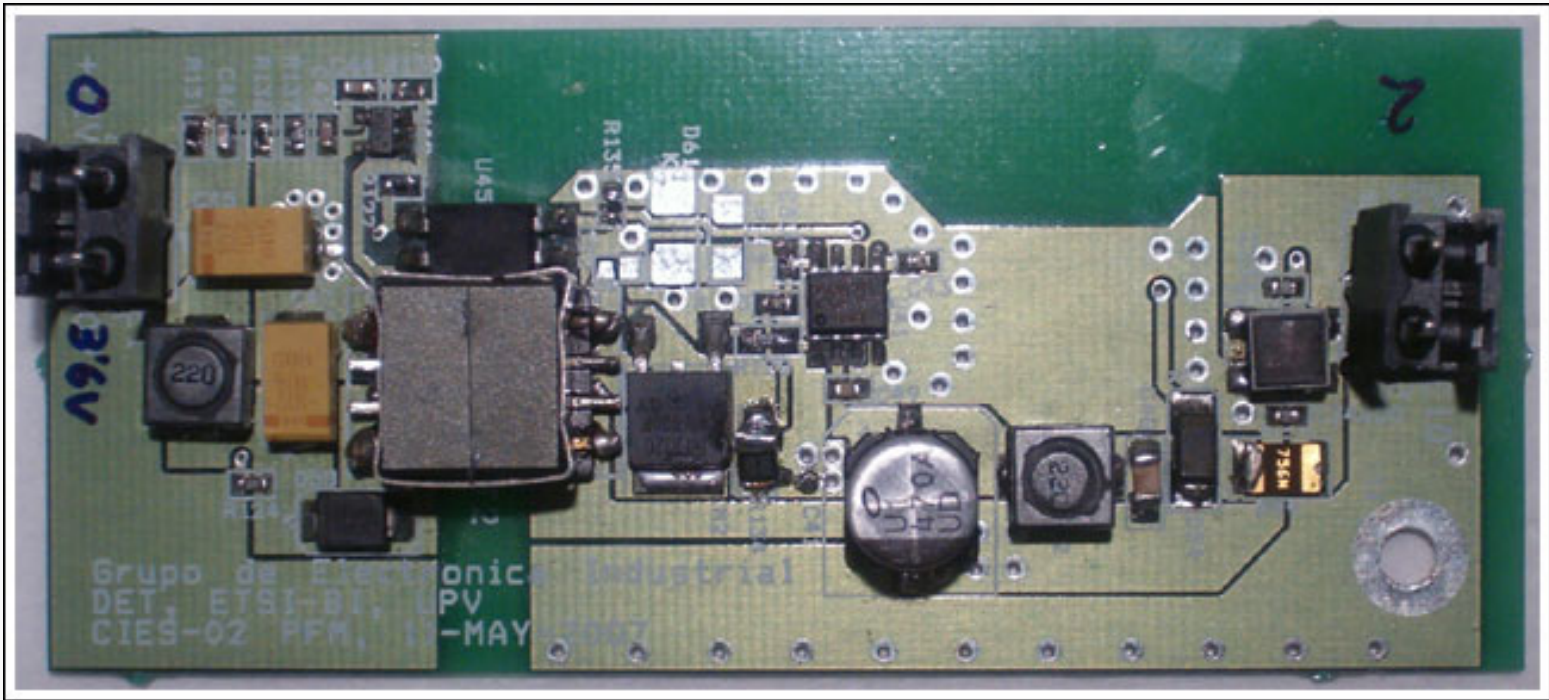

[More detailed image](#) (PDF, 4.59MB)

Figure 3. Top view of the DC-DC PFM converter prototype for wireless applications.

The prototype can be used in various wireless applications that operate in a discontinuous transmission mode. The current consumption of the modules can peak at 3A, and the maximum mean current is 1A. To reduce the current peaks and avoid the problems that they generate in the performance of the radio, the techniques described in references 2 and 3 are used. Additionally, some basic guidelines suggest that designers should use high-value capacitors that have low series resistances.

## Qualifying Design Performance

To verify the performance of the power supply, the following parameters are measured: the input voltage,  $V_{IN}$ ; the input current,  $I_{IN}$ ; the nominal output voltage,  $V_{OUT}$ ; the load current consumption,  $I_{OUT}$ ; and the efficiency of the power supply.

**Tables 3** and **4** show the measurement results, including the losses on the common-mode input filter and the losses of the protection circuitry. It is also important to remember that power supplies handling low power levels are not as efficient as power supplies handling higher loads. The higher-load power supplies are usually synchronous, which helps to reduce the losses in the active devices.

**Table 3. Current Consumption Under a No-Load State for Different Input Voltages**

$V_{IN}$ (V)	$I_{IN}$ (mA)	$V_{OUT}$ (V)	$I_{OUT}$ (A)
10.0	0.244	3.615	0
12.0	0.239	3.615	0
15.0	0.227	3.615	0

The current consumption of the power supply with a PFM control scheme has been reduced to 0.24mA. Due to component values selected, however, the control loop may oscillate during certain load conditions. To prevent self-oscillation, designers must account for the various tolerances of the components in a production environment. Thus, the values of the resistors and capacitors used in the loop must be selected with care.

Table 4 provides the values for the input and output parameters of the power supply at various load conditions. The optimum efficiency is reached at normal conditions and within the nominal load range.

**Table 4. Efficiency at Nominal Voltage for Different Loads**

$V_{IN}$ (V)	$I_{IN}$ (mA)	$V_{OUT}$ (V)	$I_{OUT}$ (A)	Efficiency (%)
12.0	0.24	3.615	0	0
12.0	61	3.615	0.14	69.14
12.0	83	3.615	0.2	72.59
12.0	121	3.615	0.3	74.69
12.0	160	3.615	0.4	75.31
12.0	200	3.615	0.5	75.31
12.0	240	3.615	0.6	75.31
12.0	281	3.615	0.7	75.04
12.0	323	3.615	0.8	74.61
12.0	367	3.615	0.9	73.88
12.0	411	3.615	1.0	73.30

The efficiency of the DC-DC converter with no load is represented as zero (**Figure 4**), because the current consumed by the wireless device in standby mode and referred to the 3.6V output side is below 140 $\mu$ A. This current is negligible when compared to the 0.24mA of the power supply's input-current consumption under no-load conditions.

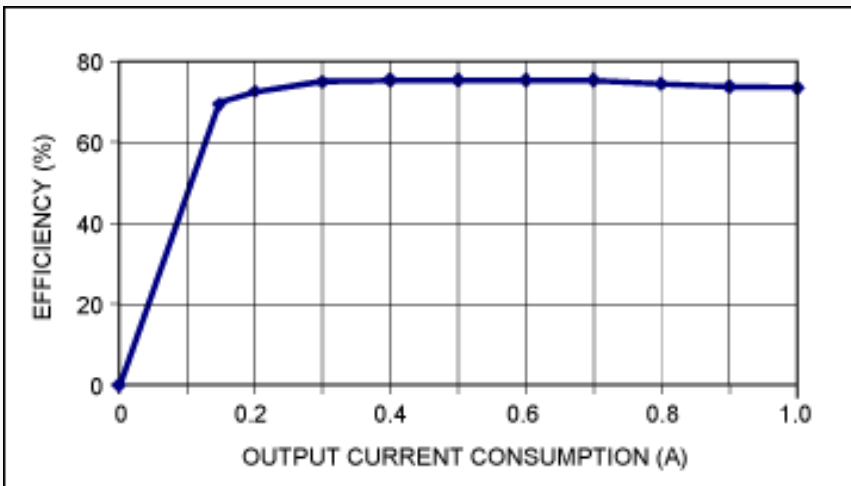


Figure 4. Efficiency of the power supply for different load conditions at the input nominal voltage (12V).

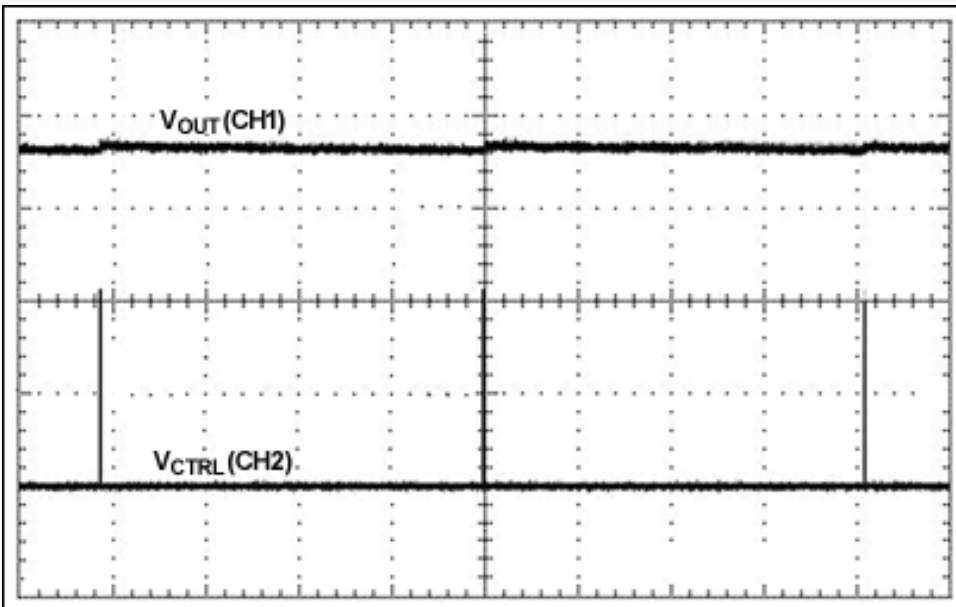


Figure 5a. Output voltage and control voltage without load (10ms/div, CH1 1V/div, and CH2 5V/div).

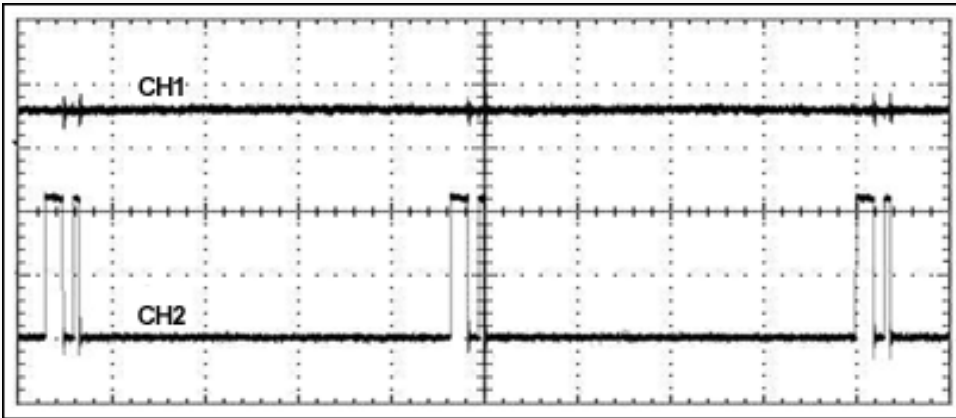


Figure 5b. Output voltage and control voltage for 0.1A load (20ms/div, CH1 1V/div, and CH2 5V/div).

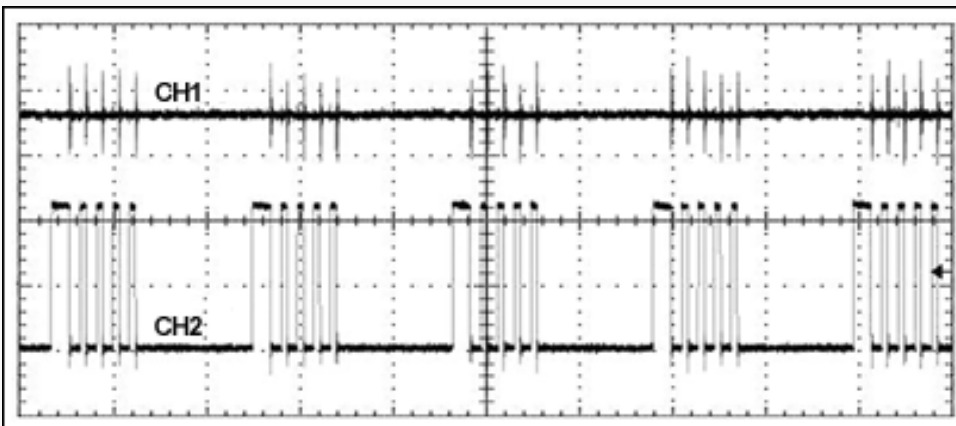


Figure 5c. Output voltage and control voltage for 0.5A load (20ms/div, CH1 1V/div, and CH2 5V/div).

The waveforms in **Figures 5a, b, c, and d** show the output voltage and control voltage for various loads; the control pulses at the gate of the switching device become more frequent as the load increases. The converter prototype shows the signals at no load, 100mA, 500mA, and 1A current loads. The scope traces graphically illustrate the operation of the PFM control scheme. The lower scope trace is scaled by 5x to make it more visible. The X axis represents the time and the Y axis the voltage.

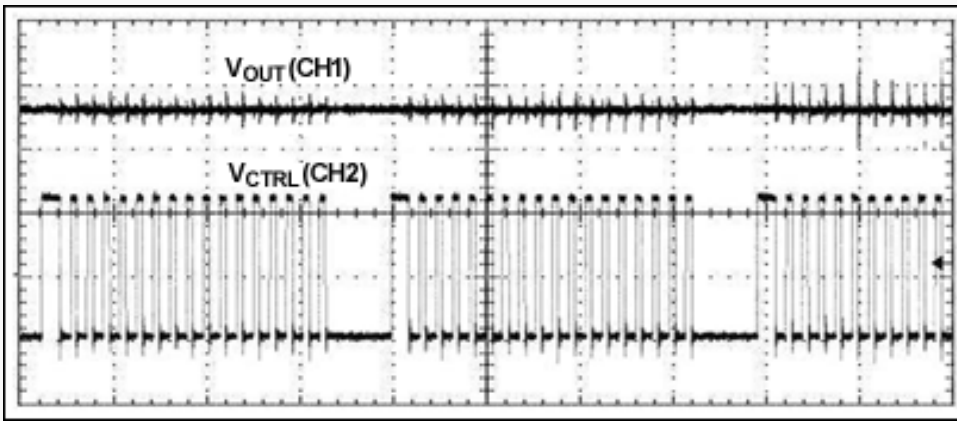


Figure 5d. Output voltage and control voltage for 1A load (20ms/div, CH1 1V/div, and CH2 5V/div).

## Summary

Initial industry surveys indicate that the best commercial isolated DC-DC converters for power supplies with low current consumption under no-load conditions typically have about 20mA minimum current consumption. With minimal effort, however, designers can use a PFM scheme to implement a low- $I_Q$ , isolated power supply that has the lowest current consumption on the market. The no-load current consumption of the power supply presented here is only 0.24mA.

## References

1. Maxim Integrated Products application note 664, "[Feedback Isolation Augments Power-Supply Safety and Performance](#)," and *EDN* magazine (June 19, 1997).
2. J. Ig. Garate, J. M. de Diego, "Consequences of Discontinuous Current Consumption on Battery Powered Wireless Terminals" [*ISIE06, Paris, France, Oct. 2006*].
3. J. M. de Diego, J. Ig. Garate, "Improvements of Power Supply Systems in Machine to Machine Modules and Fixed Cellular Terminals with Discontinuous Current Consumption" [*Digests 9<sup>th</sup> ICIT06, Mumbai, India, Dec. 2006*].

## Additional Reading

1. I. Haroun, I. Lambadiris, R. Hafez, "RF System Issues in Wireless Sensor Networks," *Microwave Engineering Europe* (Nov. 2005), pp. 31–35.
2. J. P. Joorsring, "Power dissipation could limit smartphone performance," *Microwave Engineering Europe* (Apr. 2006), comment p. 9. Available at: [www.mwsee.com](http://www.mwsee.com).
3. "MAX1649/MAX1651, 5V/3.3V or Adjustable, High-Efficiency, Low-Dropout, Step-Down DC-DC Controllers," Maxim Integrated Products Data Sheet, 19-0305; Rev 2; 9/95.
4. "MAX1771, 12V or Adjustable, High-Efficiency, Low  $I_Q$ , Step-Up DC-DC Controller," Maxim Integrated Products Data Sheet, 19-0263; Rev 2; 3/02.
5. J. Ig. Garate, J. M. de Diego, J. Monsalve, "Ultra Low Input Current Consumption Power Supplies" [*ISIE07, Vigo, Spain, Jun. 2006*].
6. J. Ig. Garate, J. M. de Diego, J. Monsalve, "Sistemas de transmisión discontinua. FAC aisladas y de muy bajo consumo en vacío," *Mundo Electrónico* (Oct. 2007), pp. 38–45.
7. R. W. Erickson, *Fundamentals of Power Electronics*, 1<sup>st</sup> Ed. (Chapman and Hall, New York, 1997).
8. B. Arbetter, R. Erickson, and D. Maksimovic, "DC-DC converter design for battery-operated systems," *Proceedings of IEEE® Power Electronic Specialist Conference* (1995), pp. 102–109.
9. B. Sahu and G. A. Rincora, "A Low Voltage, Non-Inverting, Dynamic, Synchronous Buck-Boost Converter for Portable Applications," *IEEE Transactions on Power Electronics*, vol. 19, no. 2 (Feb. 2004), pp. 443–452.
10. G. A. Rincora and P. E. Allen, "A Low-Voltage, Low Quiescent Current, Low Drop-Out Regulator," *IEEE Journal of Solid-State Circuits*, vol. 33, no. 1 (Jan. 1998), pp. 36–44.
11. D. Maksimovic, "Power management model and implementation of power management ICs for next generation wireless applications," *Tutorial Presented at the International Conference on Circuits and Systems [ISCAS, 2002]*.
12. *Data Acquisition Linear Devices Databook*. Vol. 3, National Semiconductor Corporation (1989).
13. "TPS62110 TPS62111 TPS62112, 17-V, 1.5-A, Synchronous Step-Down Converter," Texas Instruments Incorporated, SLVS585–JULY 2005 (2006).

Bourns is a registered trademark of Bourns, Inc.

C&D Technologies is a registered trademark of C&D Charter Holdings, Inc.

Ferroxcube is a registered trademark of Ferroxcube International Holding B.V.

IEEE is a registered service mark of the Institute of Electrical and Electronics Engineers.

Kemet is a registered trademark of KRC Trade Corporation.

KOA Speer is a registered trademark of KOA Speer Electronics, Inc.

Murata is a registered trademark of Murata Manufacturing Co., Ltd.

ON Semiconductor is a registered service mark of Semiconductor Components Industries, LLC.

RECOM is a registered trademark of Recom International Power.

Texas Instruments is a trademark of Texas Instruments Incorporated.

TRACO is a registered trademark of Traco Electronic AG.

Vishay is a registered trademark of Vishay Intertechnology, Inc.

---

### Related Parts

MAX1649: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX1651: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX1771: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX8515A: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

---

### Automatic Updates

Would you like to be automatically notified when new application notes are published in your areas of interest? [Sign up for EE-Mail™](#).

---

Application note 4326: [www.maxim-ic.com/an4326](http://www.maxim-ic.com/an4326)

### More Information

For technical support: [www.maxim-ic.com/support](http://www.maxim-ic.com/support)

For samples: [www.maxim-ic.com/samples](http://www.maxim-ic.com/samples)

Other questions and comments: [www.maxim-ic.com/contact](http://www.maxim-ic.com/contact)

---

AN4326, AN 4326, APP4326, Appnote4326, Appnote 4326

Copyright © by Maxim Integrated Products

Additional legal notices: [www.maxim-ic.com/legal](http://www.maxim-ic.com/legal)