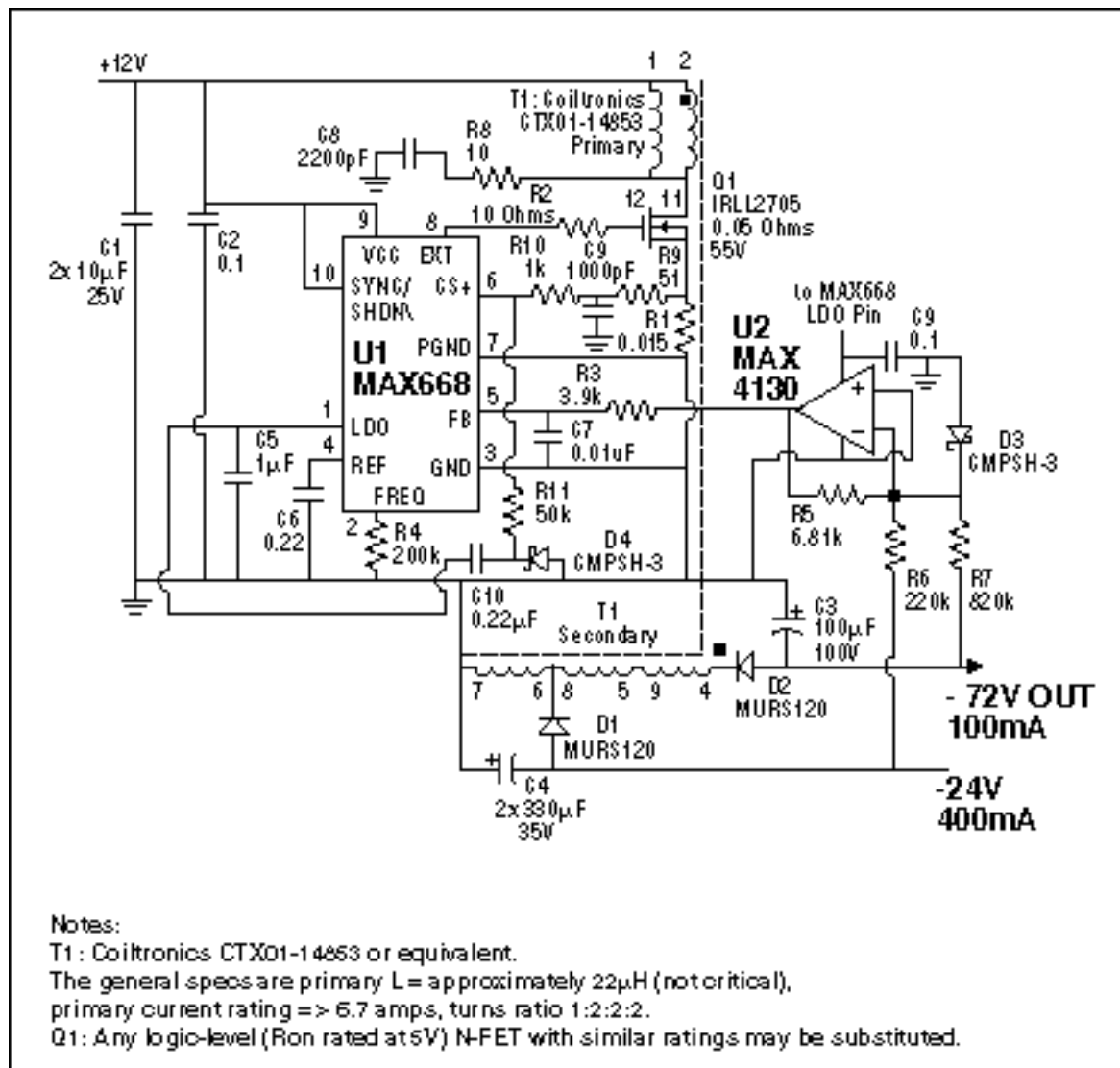


APPLICATION NOTE 436

Extending Soft-Start

Additional Information:

- [Quick View Data Sheet for the MAX668](#)
- [Quick View Data Sheet for the MAX4130](#)
- [Technical Support: Power](#)



This circuit uses the MAX668 and a transformer (which will need about a 1:2:2:2 turns ratio) to make a flyback converter. The op amp inverts the feedback from both negative output voltages.

In systems where cards are hot-plugged, it is desirable sometimes to extend the soft-start period beyond the time provided in the IC in order to control the surge current at turn-on. The circuit above uses four external components to extend the soft-start period of the MAX668 (the technique also applies to the MAX1856 inverting transformer flyback controller).

C5 is a bypass capacitor for LDO and part of the standard circuit. R1 is the current-sense resistor. R9 and C9 filter the switching noise from the current-sense signal. In normal operation, the LDO output is 5V. The switching frequency is set to 250kHz, and the internal soft-start is 1024 clock cycles, or 4msec.

R10 and R11 are added to force the current-sense input, CS+, into current limit (+100mV). C10 is the timing capacitor that works with R10 to decrease the extra voltage applied to CS+ over a period of time. As the extra voltage decreases, the allowed current limit increases. Therefore, in this example, the current limit is increased from zero to 90% of full scale over a 33msec period ($3 \times R10 \times C10$). The soft-start period is modified by changing C10. When power is removed, D4 resets the voltage on C10.

Application Note 436: www.maxim-ic.com/an436

More Information

For technical support: www.maxim-ic.com/support

For samples: www.maxim-ic.com/samples

Other questions and comments: www.maxim-ic.com/contact

Automatic Updates

Would you like to be automatically notified when new application notes are published in your areas of interest?

[Sign up for EE-Mail™.](#)

Related Parts

MAX4130: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX668: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN436, AN 436, APP436, Appnote436, Appnote 436

Copyright © by Maxim Integrated Products

Additional legal notices: www.maxim-ic.com/legal