

APPLICATION NOTE 4617 ADC Input Translator

By: Paul Ward

Abstract: Using resistor dividers to scale the differential inputs and a stable voltage reference to offset the inputs, this circuit enables an ADC with 0V to 5V input range (MAX1402) to accept inputs in the range +10.5V to -10.5V.

This design idea appeared in the August 5, 2008 issue of *EE Times* magazine.

Many high-accuracy analog-digital converters require input levels between 0.0V and 5.0V. As an example, the [MAX1402](#) (an 18-bit multi-channel sigma-delta ADC) measures the difference between two inputs. In a typical single-ended application, it compares an input voltage with a fixed reference voltage such as 2.500V: for $ADC_{IN} = 0V$ the digital output represents $0V - 2.5V = -2.5V$, for $ADC_{IN} = 2.5V$ the output represents $2.5V - 2.5V = 0V$, and for $ADC_{IN} = 5V$ the output represents $5V - 2.5V = 2.5V$. Thus, the digital output range corresponding to ADC_{IN} values between 0V and 5V is $\pm 2.5V$.

The circuit of **Figure 1** converts an input signal in the range $\pm 10.5V$ to the input range of the MAX1402 ADC (0V to 5V). Two of the ADC channels (IN1 and IN2 in this case) are configured for either full differential or precision single-ended measurements. Resistor dividers R1 and R2 scale the inputs, and a stable source of 3.28V offsets the inputs. As a result, the ADC input is centered at 2.50V when the measurement inputs are grounded. (That is, the ADC digital output is zero when $V_{IN} = 0V$.)

Precision component values maintain the ADC's 16-bit accuracy.

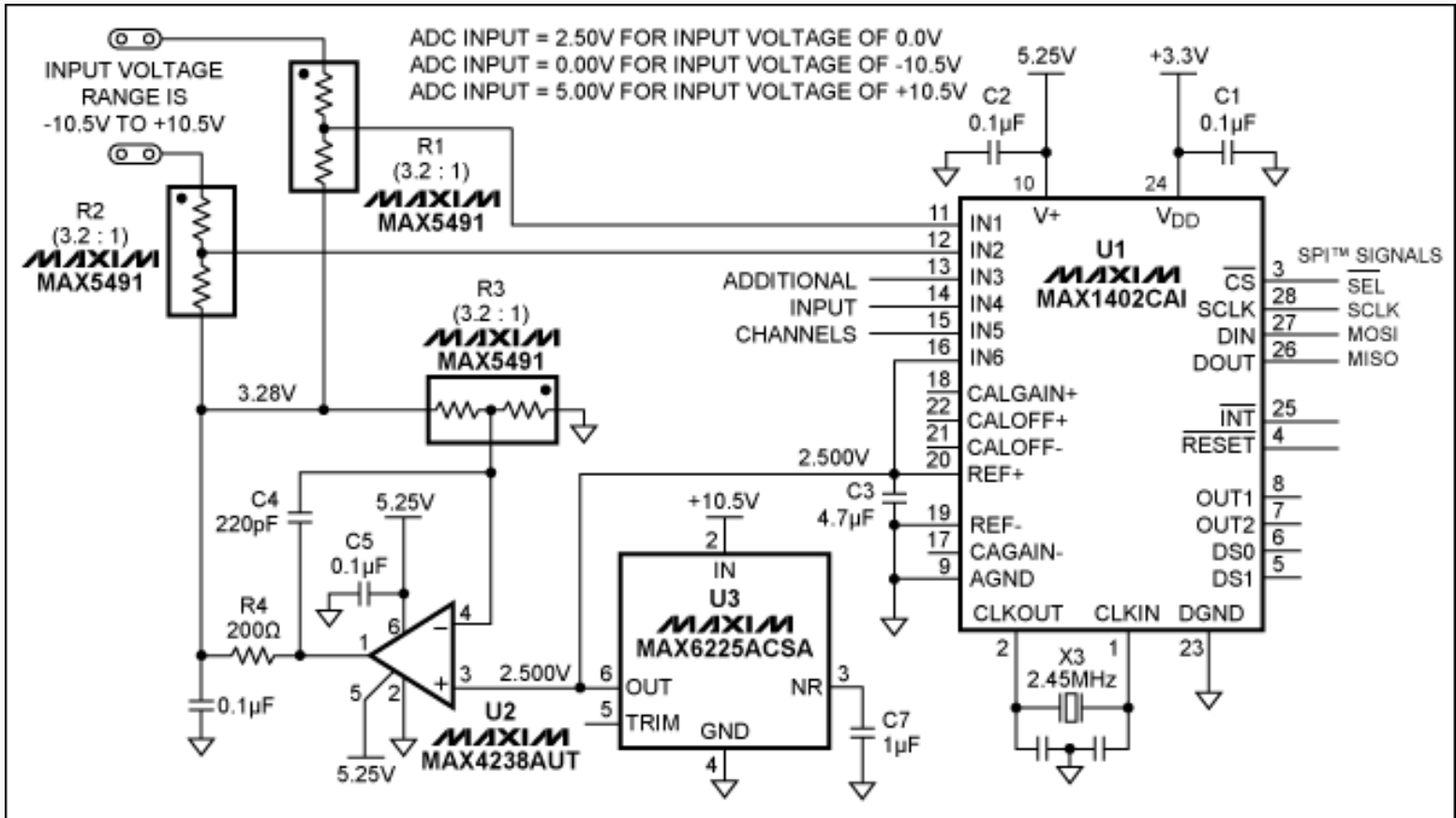


Figure 1. This circuit enables an ADC with input range of 0V to 5V (single-ended or differential) to accept inputs in the range $\pm 10.5V$.

Configuring the MAX1402 for differential measurements allows it to measure the voltage difference between IN1 and IN2. These inputs accept voltages anywhere in the $\pm 10.5V$ range, and the internal programmable-gain amplifier (PGA) is available to increase the resolution for low-level signals. A gain of four, for example, enables the ADC to resolve a $\pm 2.625V$ input signal

with 16-bit resolution.

To make single-ended measurements you can configure the inputs as two separate channels, and compare them to a 2.50V reference voltage attached to IN6. Or, for higher precision, you can configure the ADC for differential inputs, with one channel acting as a ground-sense input.

The resistor divider ratio can be altered to accommodate different input ranges, but the same ratio is needed in the circuit that generates the offset voltage. A ratio of 5:1, for example, would yield an input range of $\pm 15.0V$ and an offset voltage of 3.00V. To calibrate the system, simply record the output value with inputs grounded and with a known input voltage. Those two values let you calculate the offset and gain factors for each input range.

SPI is a trademark of Motorola, Inc.

Related Parts

MAX1402: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX4238: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX5491: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX6225: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

Automatic Updates

Would you like to be automatically notified when new application notes are published in your areas of interest? [Sign up for EE-Mail™](#).

Application note 4617: www.maxim-ic.com/an4617

More Information

For technical support: www.maxim-ic.com/support

For samples: www.maxim-ic.com/samples

Other questions and comments: www.maxim-ic.com/contact

AN4617, AN 4617, APP4617, Appnote4617, Appnote 4617

Copyright © by Maxim Integrated Products

Additional legal notices: www.maxim-ic.com/legal