

APPLICATION NOTE 675

Powering Portable CPU Cores

Providing electrical power for CPUs and other high-density logic has never been easy, though it appeared for awhile that technology would eventually reduce the power needed for computing tasks. Although technology advances have been rapid, the ever-increasing demand for computing power seems to absorb all improvements and call for more. This appetite for power is especially apparent in notebook computers, whose battery-life extensions have been incremental at best, despite enormous growth in the computing power available per watt.

Whether this performance plateau results from a need to keep pace with technology or vice versa, the need for higher supply current in portable systems is forcing designers to become familiar with new power-supply technologies. This article explores some of these new technologies.

Shrinking geometries have consistently driven down the supply voltages for CPUs, DSPs, and other large-scale logic devices. Currently in the +1.5V to +2.5V range, these voltages should soon reach 1V. Efficient generation of voltages this low can be a problem, especially for output currents of 10A and up.

As for most electronic designs, an effective power supply must reconcile numerous conflicting goals including cost and component count, efficiency and thermal behavior, circuit size, and transient performance (response to load steps, etc.). Battery life is an issue for portable (battery-powered) systems only, but waste heat (and therefore efficiency) is a major concern for both battery- and AC-powered systems.

Tighter Load Regulation + Faster Response = A Losing Battle

Today's CPU cores require very tight load regulation. Until recently, the major CPU makers demanded exactly that. But the supply current and clock frequency rise as supply voltages fall, and that places acute demands on the power supply—especially with regard to load-step behavior. The growing difficulty and cost of meeting these ever-tighter performance limits has motivated a rethinking of power-supply design. As just one consequence of higher load currents and larger load transients, the capacitor "farms" that sprout up around a processor add size and cost to a design.

These issues, and the fact that even the fastest switch-mode regulators cannot handle the instantaneous output drop caused by a sudden load step, have forced a change of thinking (and specifications). Output capacitors must do all the work in coping with a step response at the speed of today's CPUs. Furthermore, the tighter load-regulation specs that result in higher open-loop gain require more output capacitance to maintain stability. Thus, it became clear that some way of relaxing the demands of load regulation would pay off generously in reduced component count and in other ways as well.

The response of a typical DC-DC converter to a load step (**Figure 1**) has five basic elements:

1. An instantaneous drop, whose magnitude equals the increase in the load-current step multiplied by the output capacitors' equivalent series resistance (ESR).
2. After the instantaneous drop, there may be a droop before the DC-DC converter responds, in which capacitor voltage falls as the capacitor supplies load current.
3. A voltage-recovery interval, as the inductor switches on to source load current and replenish the output capacitance.
4. An "ESR step-up" as the load is removed (reversing the effect of the instantaneous drop).
5. Some overshoot, as energy stored in the first inductor pulse (after the load falls) is transferred to the output capacitance.

Elements 2, 3, and 5 can be minimized with careful design and a judicious selection of the DC-DC controller. But

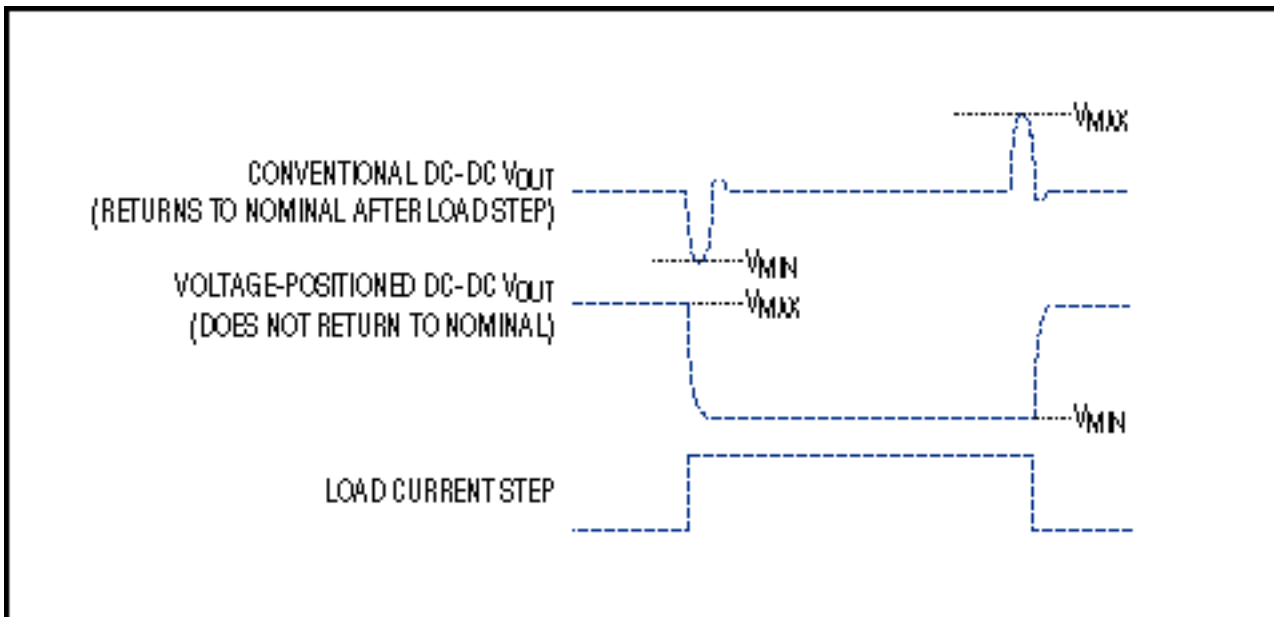


Figure 2. Because voltage-positioned regulators don't attempt to restore the output voltage to a centered "nominal" after each load step, they allow larger transient excursions. This extra margin reduces power consumption and the output-capacitor count as well.

These considerations have led to a new type of specification for CPU power supplies (see the gray box in Figure 1). The nominal voltage is 1.6V, but load-dependent droop can pull it down by 7.5% (quite sloppy by current CPU standards). It can also rise by 7.5% (short-term pulses only) when the load drops from full to zero. Output voltage in the steady state must not exceed 1.65V including noise and ripple. These numbers help minimize the capacitor count while allowing major gains in battery life and heat reduction.

To take full advantage of the wider limits for CPU power supplies, you can define a voltage/load profile for a given supply. This characteristic lets you implement a controlled form of load rejection—sometimes called voltage positioning—in which the output voltage is positioned as a function of load current. Voltage positioning allows the output to droop, and does not waste energy and money trying to prop it back up. Instead, the output is set to fall in a defined way as the load current increases. This approach offers a more graceful response to transient problems than the brute force approach (which offers limited benefits yet requires more capacitance and more speed from the DC-DC converter).

Voltage positioning capability can be added to many DC-DC controllers with no more than three resistors (**Figure 3**). R4 and R5 add a small positive offset to the set output voltage, raising it from a nominal 1.6V (in this example) to 1.62V. R6 (R_{VP}) is in series with the output, matching the worst-case ESR of the output capacitor. The effect of R_{VP} is to insert a defined, load-dependent voltage drop.

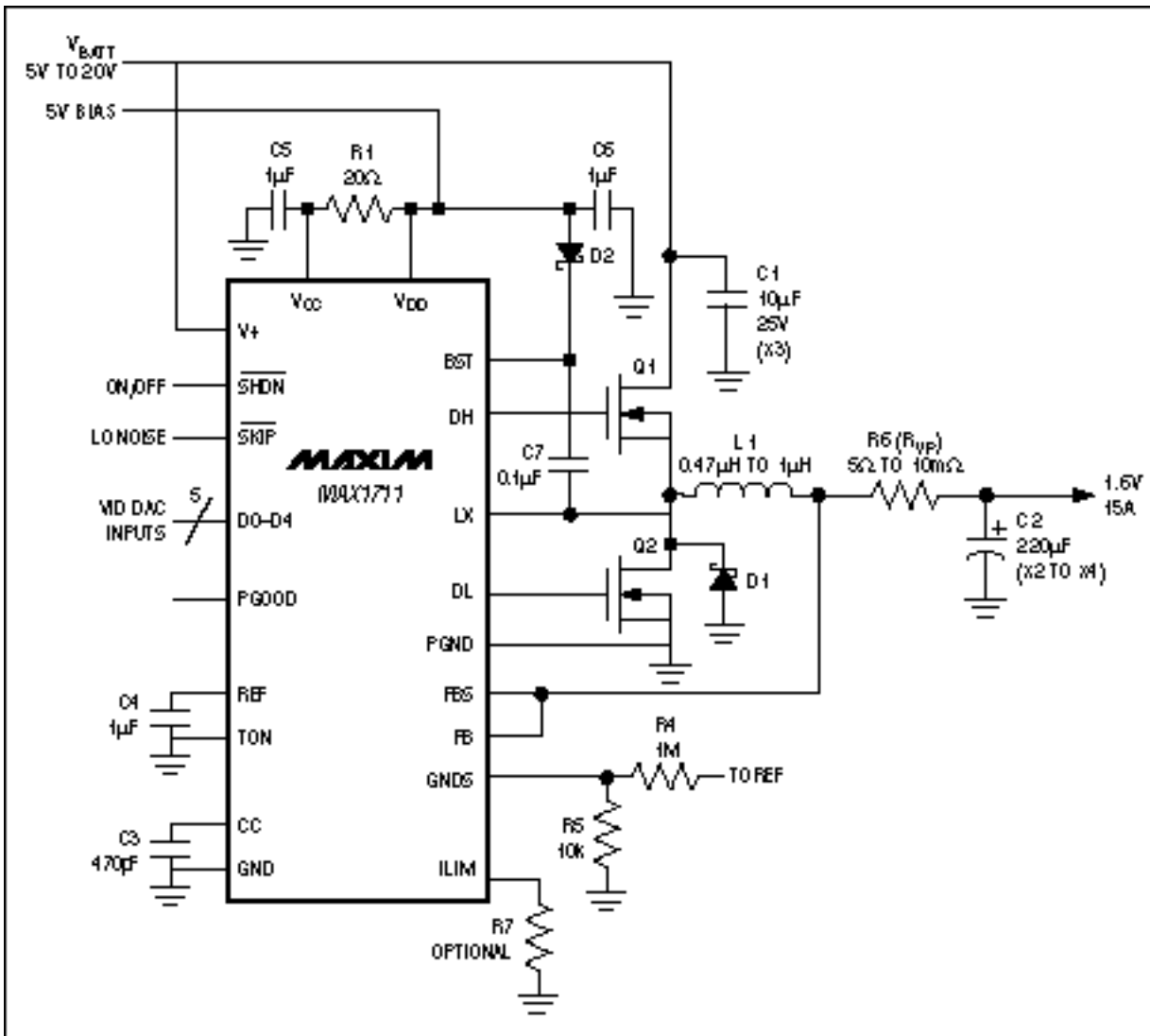


Figure 3. This efficient 15A regulated supply easily converts to a voltage-positioned design with the addition of three resistors: R4, R5, and R6 (R_{VP}).

$I_{OUT}(A)$	C1(μF)	L1(μH)	R6(R_{VP} , mohm)	R7	C2(μF)	Q1	Q2
7	(2) 10	1	10	$I_{LIM} = V_{CC}$	(2) 220	IRF7807	IRF7805
10	(3) 10	0.68	8	$I_{LIM} = V_{CC}$	(3) 220	IRF7811	IRF7809
12	(3) 10	0.47	7	220 k Ω	(4) 220	IRF7811	IRF7809
15	(4) 10	0.47	5	210 k Ω	(4) 220	IRF7811	IRF7809*

C1 = Ceramic Capacitor, C2 = Panasonic SP series: EEFUEOE221R.

*For continuous 15A load, use (2) IRF7811 or (2) IRF7805 due to thermal limitation of IR7809.

If R_{VP} matches the filter capacitor's ESR, the output falls by the initial load-step drop ($ESR \times I_{LOAD}$), and remains at that level for as long as the load remains unchanged. Reducing the load causes the voltage level to rise by ($\Delta I \times ESR$). After a brief transient pulse from the last inductor discharge and before the controller's 100ns response (but within the allowed 7.5% limit), the dc level again remains at a level defined by the no-load voltage (1.62V in this case) minus $I_{LOAD} \times R_Z$. See **Figure 4**.

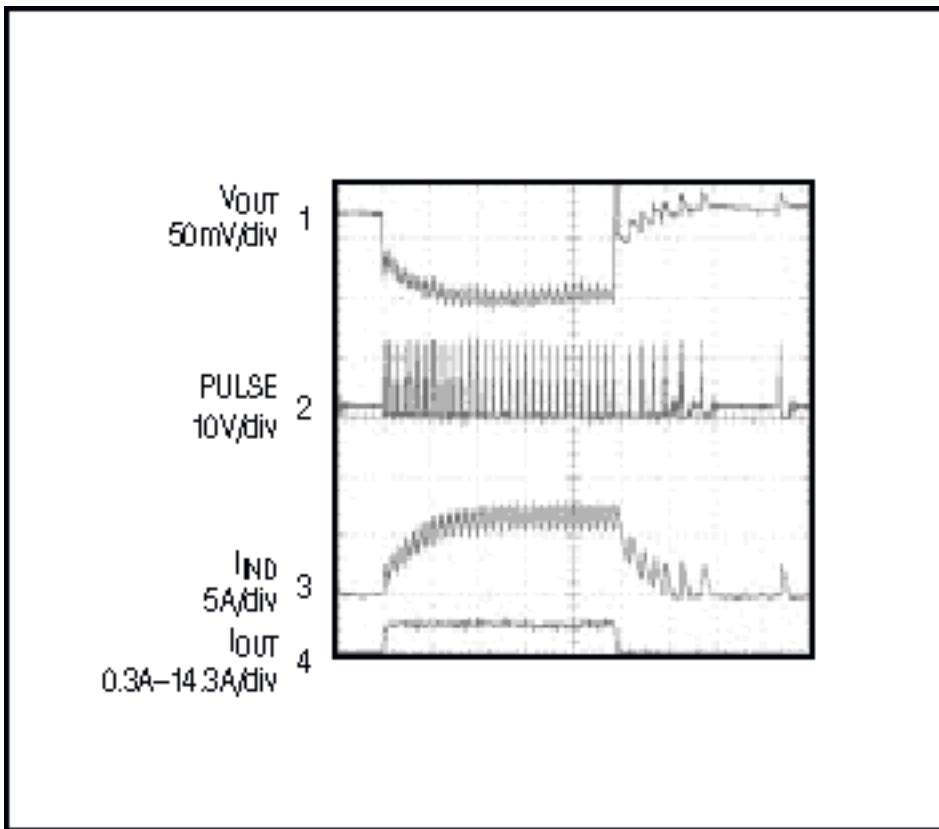


Figure 4. The step response of Figure 3's circuit illustrates the advantage of a voltage-positioned output.

Adding $5\text{m}\Omega$ in series with the output reduces efficiency. However, it also reduces the CPU's operating voltage under heavy load, which lowers power dissipation and improves battery life. Compared with conventional (nonpositioned) regulators, a voltage-positioned design lowers the CPU dissipation by 1.38W and lowers the overall power consumption by 0.4W (Figures 5, 6).

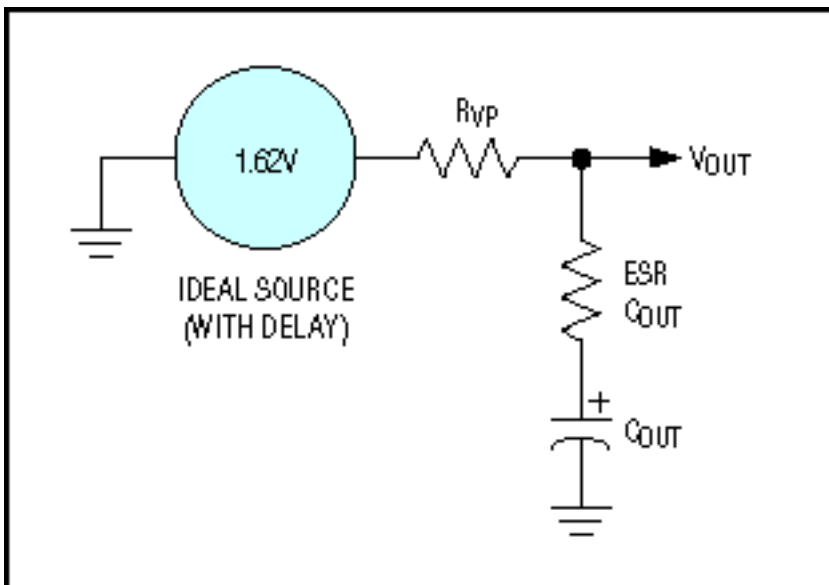


Figure 5. This simplified model illustrates the basics of voltage positioning. The ideal "square-wave" voltage response to a load step (Figure 2) occurs when R_{VP} equals ESR (the effective series resistance of C_{OUT}).

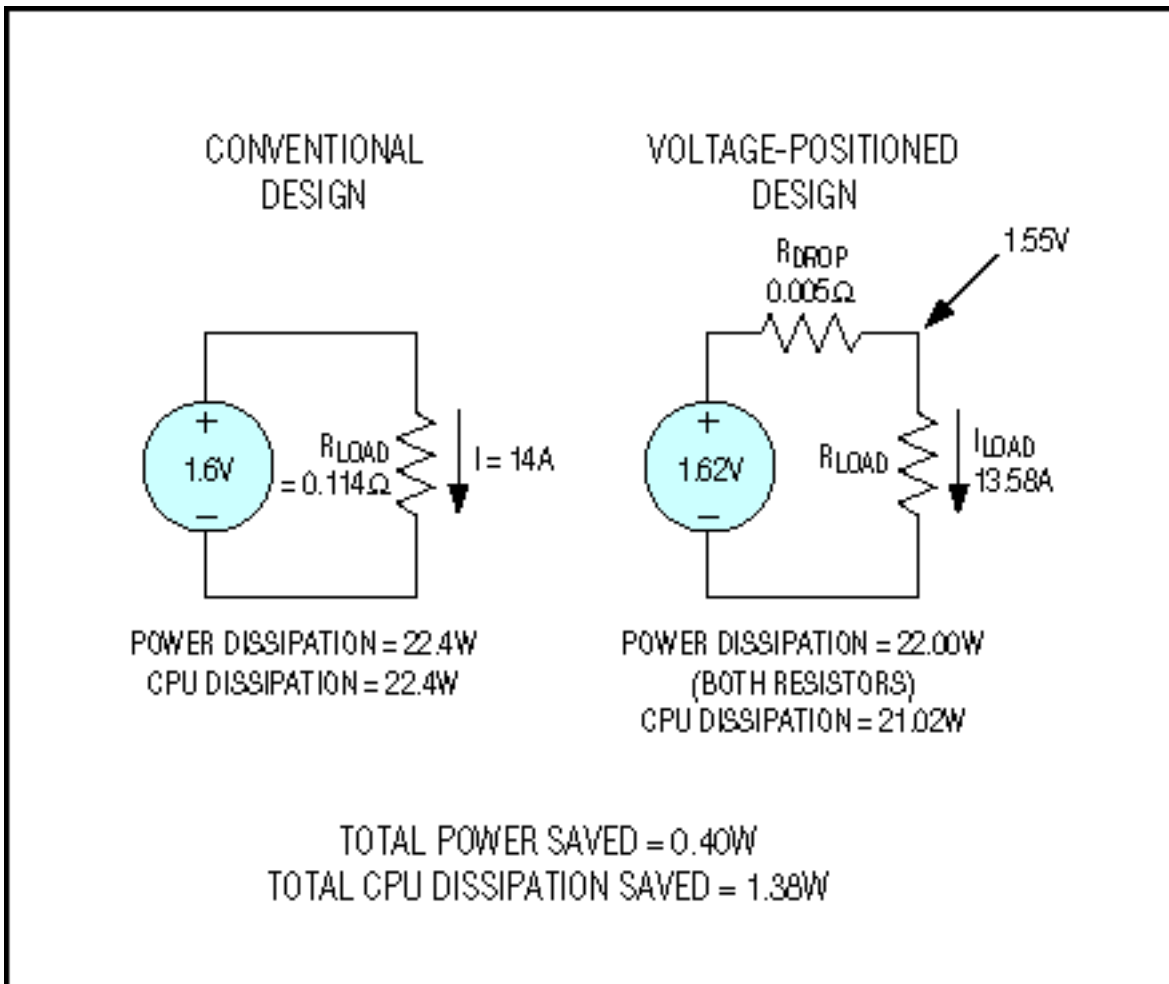


Figure 6. Despite added output resistance that reduces the conversion efficiency, a voltage-positioned design reduces power dissipation in the power supply and within the CPU.

Effective Efficiency

Because this improvement comes at the expense of conversion efficiency, it may be helpful to propose a new term that compares a voltage-positioned circuit with a conventional (nonpositioned) one. This term, "effective efficiency," is the efficiency required in a nonvoltage-positioned design to equal the performance of a voltage-positioned design.

To determine the effective efficiency of a voltage-positioned regulator, first measure its efficiency in the conventional way $[(V_{OUT} \times I_{OUT}) / (V_{IN} \times I_{IN})]$, then model the load as a resistance for each efficiency data point ($R_{LOAD} = V_{OUT} / I_{OUT}$). Next, calculate the output current for each R_{LOAD} data point, using the nonpositioned output voltage ($I_{NP} = V_{NP} / R_{LOAD}$, where $V_{NP} = 1.6V$ in this case). Effective efficiency is then calculated at each I_{NP} data point, as the nonpositioned power output ($V_{NP} \times I_{NP}$) divided by the measured voltage-positioned power input ($V_{OUT} \times I_{OUT}$). Note that an effective efficiency exceeding 100% is mathematically possible, but has yet to be achieved.

Figure 7 shows how dramatic this improvement can be for a typical CPU power supply. To match the benefits derived from voltage positioning, a conventional design at full load would need an efficiency improvement of nearly 8%.

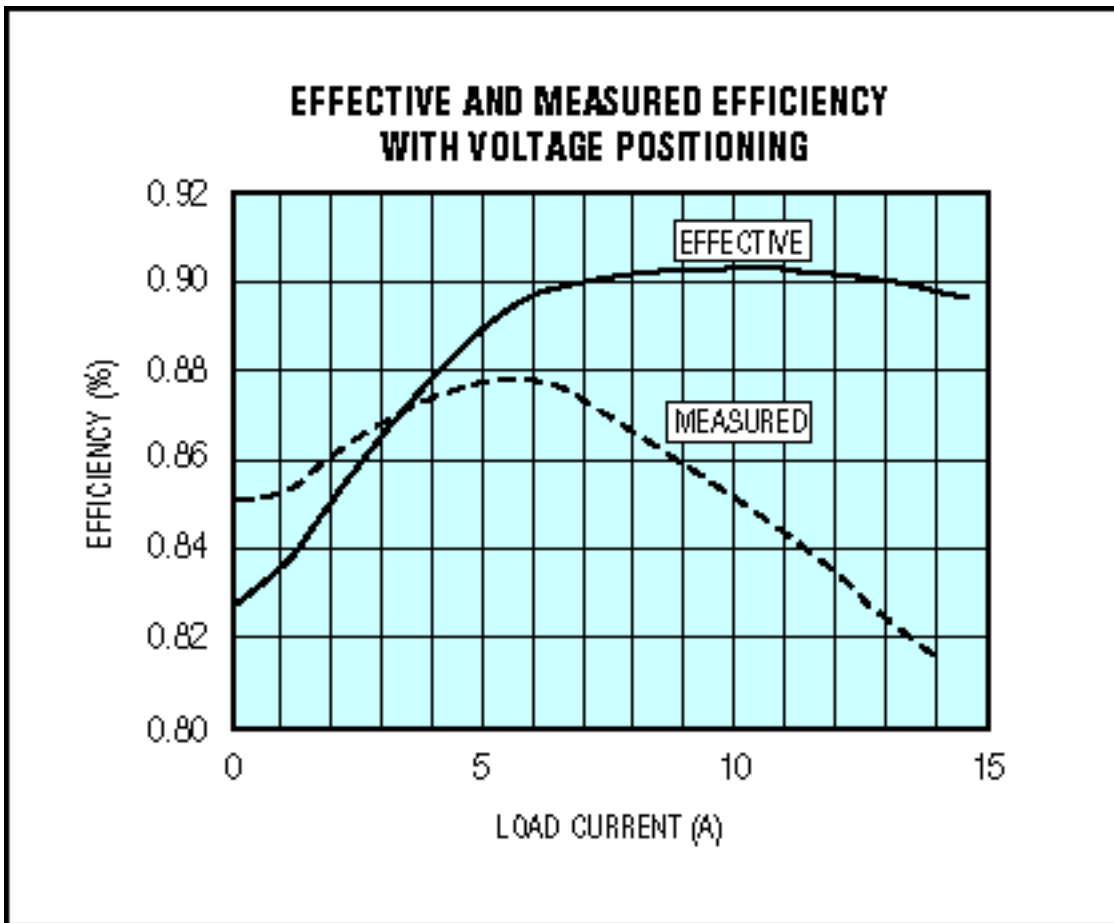


Figure 7. These plots show an 8% advantage for the voltage-positioned CPU power supply at full load. A conventional design would need 90% conversion efficiency to match the 82% efficiency of a voltage-positioned design delivering 14A.

Application Note 675: <http://www.maxim-ic.com/an675>

More Information

For technical questions and support: <http://www.maxim-ic.com/support>

For samples: <http://www.maxim-ic.com/samples>

Other questions and comments: <http://www.maxim-ic.com/contact>

AN675, AN 675, APP675, Appnote675, Appnote 675

Copyright © by Maxim Integrated Products

Additional legal notices: <http://www.maxim-ic.com/legal>